



College of Engineering, Science and Technology (CEST)

School of Electrical & Electronic Engineering

FINAL EXAMINATION 2013

Program	Diploma in Electrical & Electronics Engineering
Semester	1
Unit Code	EEE503
Unit Title	Analogue Electronics 2B
Date of Examination	Refer ETT
Time	Refer ETT
Venue	Refer ETT
Duration	2 hours (Extra 10 minutes allowed for reading the paper)
Maximum Marks	100

Instructions:

1. Attempt ALL questions in this examination booklet.
2. Write your answers legibly in the answer booklet.
3. Write your student identification number on each page used.
4. There are five (5) questions in total worth 20 marks each.

GOOD LUCK!

Question 1 - 20 marks

A. Fill in the blanks

10 marks

Description

Component

1. A fixed gain monolithic power amplifier _____ (1 mark)
2. In the power amplifier circuit, these transistors provide the input buffering _____ (2 marks)
3. These 2 resistors provide dc paths to ground for the base currents _____ (2 marks)
4. These transistors act as a current booster _____ (2 marks)
5. Name the transistor that sinks the additional load current _____ (1 mark)
6. State the percentage of distortion at which peak clipping begins _____ (2 marks)

- B. With the aid of a diagram, explain the importance of utilizing heat-sinks in electronic circuits?**

10 marks

Question 2 – 20 marks

- A. It is required to design a tuned amplifier having $f_o = 1\text{MHz}$, 3dB bandwidth = 10kHz and centre-frequency gain = -10V/V. The FET available has at the bias point $g_m = 5\text{mA/V}$ and $r_o = 10\text{k}\Omega$. The output capacitance is negligibly small. Determine the values of:**

- i. R_L (1 mark)
- ii. C_L and (2 marks)
- iii. L (2 marks)

- B. Define the following terms:**

- i. Skirt selectivity (1 mark)
- ii. Narrow-band (1 mark)
- iii. Closed loop gain (1 mark)

- C. State two (2) applications of coupling capacitors (2 marks)**


- D. Feedback can be either negative or positive. State five (5) properties when designing amplifiers that would bring about negative feedback. (5 marks)**

- E. The manufacturer specifies that for ambient temperatures below 25°C the LM380 can dissipate a maximum of 3.6W. This is obtained under the condition that its dual-in-line package be soldered onto a PCB in close thermal contact with 6sq. inches of 2-ounce copper foil. Above the ambient temperature of 25°C, the thermal resistance is $\Theta_{JA} = 35^\circ\text{C/W}$. T_{Jmax} is specified to be 150°C. Find the maximum power dissipation possible if the ambient temperature is to be 50°C. (5 marks)**

Question 3 – 20 marks

- A. i) Draw and fully label the Cathode-Ray-tube. (5 marks)**
 ii) Describe the operation of each part of the tube drawn in part (i) (5 marks)

B. Consider this circuit

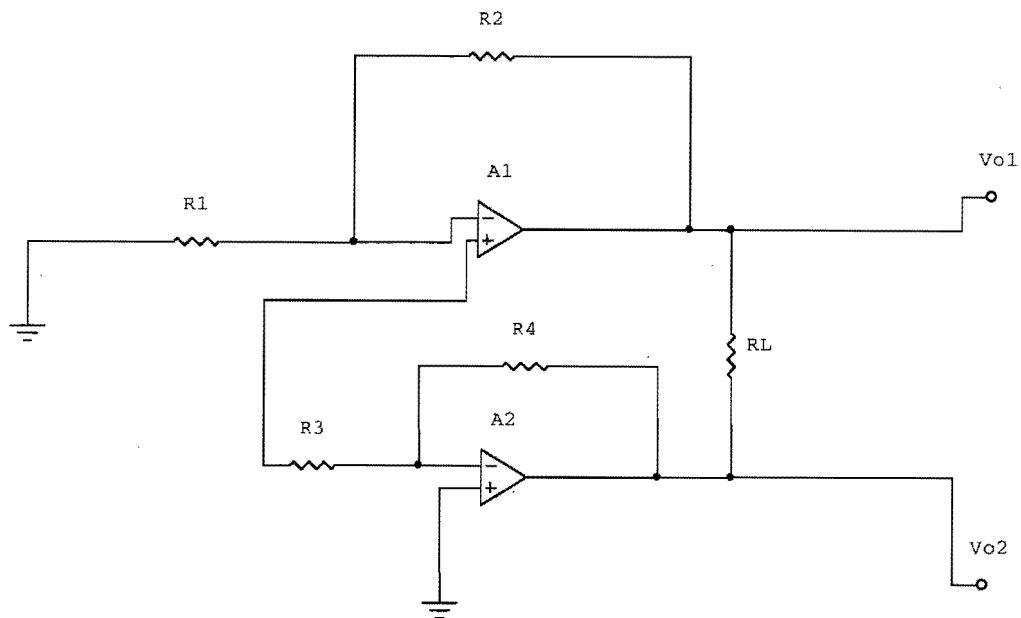

The component values are: $R_1 = R_3 = 10\text{k}\Omega$, $R_2 = 5\text{k}\Omega$, $R_4 = 15\text{k}\Omega$, and $R_L = 8\Omega$. Find the

- i) voltage gain and (2 marks)
- ii) the input resistance. (2 marks)
- iii) The power supply used is $\pm 18\text{V}$ and if v_i is a 20-V peak-to-peak sine wave, what is the peak-to-peak output voltage? (2 marks)
- iv) What is the peak load current? (2 marks)
- v) What is the load power? (2 marks)

Question 4 – 20 marks

A. Design the RC elements of a Wien Bridge oscillator that oscillates at $f_o = 25\text{kHz}$ and clearly state all assumptions and justifications. Construct and clearly label the Wien Bridge circuit using an op-amp. (5 marks)

B. Design an RC Phase-shift oscillator that will oscillate at 100Hz. (Take $C = 0.5\mu\text{F}$). (2 marks)


C. Draw and label the basic oscillator block diagram and explain how the oscillator works. (3 marks)

D. State the Barkhausen Criterion both mathematically and theoretically. (4 marks)

E. Describe the operation of a monostable op-amp circuit. Clearly label the circuit diagram and indicate both input and output waveforms. (6 marks)

Question 5 – 20 marks

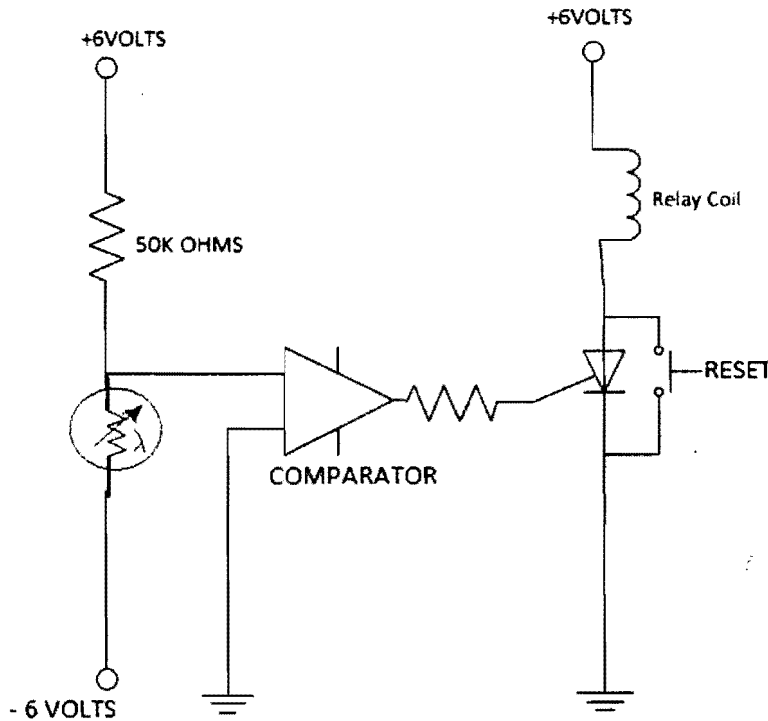- A. With the aid of a fully labelled construction diagram of a liquid-crystal display, explain the components that make-up the LCD. (8 marks)
- B. Explain the two (2) fundamental ways in which liquid-crystals are used to control properties of light and thereby alter its appearance. (4 marks)
- C. For the circuit shown below,



when the photoconductive cell is illuminated by a light beam, it has a resistance of $20\text{k}\Omega$. The dark resistance is $100\text{k}\Omega$. Show that the relay is de-energized when the cell is illuminated and energized. (4 marks)

- D. State a distinguishing feature of the following components:
 - i) Light-emitting diode (LED) (1 mark)
 - ii) Optoisolator (1 mark)
 - iii) Photodiode (1 mark)
 - iv) Solar cells (1 mark)

END.