



COLLEGE OF ENGINEERING, SCIENCE AND TECHNOLOGY

SCHOOL OF ELECTRICAL AND ELECTRONICS  
ENGINEERING

PENSTER 1/2014

EEE413 – ANALOGUE ELECTRONICS 1A

SOLUTION

ID Number: \_\_\_\_\_

**Section A**

**Multiple Choice**

**[30 Marks]**

Circle the letter of your **Best** choice

1	A	B	C	D
2	A	B	C	D
3	A	B	C	D
4	A	B	C	D
5	A	B	C	D
6	A	B	C	D
7	A	B	C	D
8	A	B	C	D
9	A	B	C	D
10	A	B	C	D
11	A	B	C	D
12	A	B	C	D
13	A	B	C	D
14	A	B	C	D
15	A	B	C	D
16	A	B	C	D
17	A	B	C	D
18	A	B	C	D
19	A	B	C	D
20	A	B	C	D
21	A	B	C	D
22	A	B	C	D
23	A	B	C	D
24	A	B	C	D
25	A	B	C	D
26	A	B	C	D
27	A	B	C	D
28	A	B	C	D
29	A	B	C	D
30	A	B	C	D

NB: Attach this sheet with the answer booklet.

**Question 1****Operational Amplifier (OP-AMPS)****[20 Marks]**

- a. Complete the table given below about the four main properties of real and ideal op-amp.

Properties	Ideal	Real
$A_d$	<b>Infinity</b>	<b>200,000</b>
CMRR	<b>Infinity</b>	<b>90dB</b>
$R_{in}$	<b>Infinity</b>	<b>2M</b>
$R_{out}$	<b>0</b>	<b>75</b>

(4 marks)

b.  $CMRR = 20 \text{ Log } A_d/A_c \text{ dB}$   
 $= 20 \text{ Log } 2000/0.2 \text{ dB}$   
 $= \underline{\underline{80 \text{ dB}}}$

(3 marks)

c. .

i.  $A_v = V_{out}/V_{in} = -R_f/R_{in}$   
 $= 100k / 10k$   
 $= 10 \text{ or } 20 \text{ dB}$

(2 marks)

ii Gain =  $-R_f/R_{in}$

$$A_1 = -10k / 1k$$

$$= -10$$

$$A_2 = -10k / 2k$$

$$= -5$$

$$\underline{\underline{V_{out} = - (10(2\text{mV}) + 5 (5\text{mV})) = - 45\text{mV}}}$$

(2 marks)

- d. 1 – ii  
 2 – i  
 3 – iv  
 4 – iii

(1 mark each = 4 marks)

e.  $I_E = V_{EE} - 0.7V/R_E$   
 $= 9 - 0.7/3.9k$   
 $= \underline{\underline{2.515\text{mA}}}$

(2 marks)

$$I_C = I_E/2$$

$$= 2.515\text{mA}/2$$

$$= \underline{\underline{1.2576\text{mA}}}$$

(1 mark)

$$\begin{aligned}
 V_C &= V_{CC} - I_C R_C \\
 &= 9 - (1.25 \times 10^{-3}) (3.9 \times 10^3) \\
 &= \underline{\underline{4.095V}}
 \end{aligned}$$

(2 marks)

**Question 2**

**BJT**



**[20 Marks]**

- a. i) low; heavily  
 ii) lower  
 iii) high; lightly

(1 mark each = 5 marks)

b. NPN

PNP

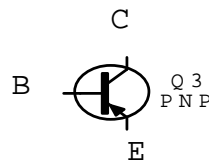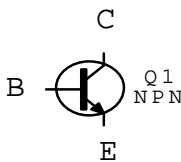

(2 marks)

- c. i) Base Bias  
 ii) Emitter Bias  
 iii) Voltage Divider Bias  
 iv) Collector – Feedback Bias (Any Three)

(3 marks)

d. i.  $V_{BE} = 0.7V$

(1 mark)

ii. 
$$\begin{aligned}
 I_B &= (V_{BB} - V_{BE})/R_B \\
 &= (5V - 0.7V)/3.9 \times 10^3 \\
 &= \underline{\underline{1.103mA}}
 \end{aligned}$$

(2 marks)

iii. 
$$\begin{aligned}
 I_C &= I_B \\
 &= 50 \times 1.103mA \\
 &= \underline{\underline{55.12mA}}
 \end{aligned}$$

(2 marks)

iv. 
$$\begin{aligned}
 I_E &= I_B + I_C \\
 &= 1.103mA + 55.128mA \\
 &= \underline{\underline{56.23mA}}
 \end{aligned}$$

(1 mark)

v. 
$$\begin{aligned}
 V_{CE} &= V_{CC} - I_C R_C \\
 &= 15 - (55.128 \times 10^{-3})(180) \\
 &= \underline{\underline{5.07V}}
 \end{aligned}$$

(2 marks)

$$\begin{aligned}
 \text{vi. } V_{CB} &= V_{CE} - V_{BE} \\
 &= 5.07 - 0.7 \\
 &= \underline{\underline{4.37V}}
 \end{aligned}$$

(2 marks)


**Question 3**

**FET**

**[20 Marks]**

a.

**JFET**

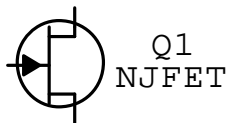


N – Channel



P- Channel

(2 marks)

**DE – MOSFET**

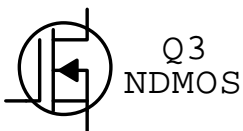


N – Channel




P – Channel

(2 marks)

**E – MOSFET**

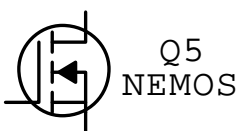

N – Channel

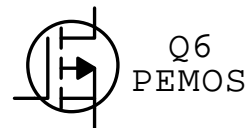

P- Channel

(2 marks)

b.  $R_{in} = |V_{GS}/I_{GSS}|$

$$\begin{aligned}
 &= 20/2 \times 10^{-9} \\
 &= \underline{\underline{10,000M}}
 \end{aligned}$$

(3 marks)

c. i) The device has a negative VGS (off), therefore is a P – Channel MOSFET. (1 mark)

$$\text{ii) } I_D = I_{DSS} \times \left(1 - \frac{V_{gs}}{V_{gs(off)}}\right)^2$$
$$I_D = 18 \times 10^{-3} \times \left(1 - \frac{-3}{-8}\right)^2$$

**I<sub>D</sub> = 11.25mA** (3 marks)

$$\text{iii) } I_D = I_{DSS} \times \left(1 - \frac{V_{gs}}{V_{gs(off)}}\right)^2$$
$$I_D = 18 \times 10^{-3} \times \left(1 - \frac{3}{-8}\right)^2$$

**I<sub>D</sub> = 24.75mA** (3 marks)

d.  $V_S = I_D \times R_S$   
 $= (5 \times 10^{-3}) (470)$   
 $= \mathbf{2.35V}$  (1 mark)

$$V_D = V_{DD} - I_D R_D$$
$$= 15 - (5 \times 10^{-3})(1 \times 10^3)$$

**= 10V** (1 mark)

$$V_{DS} = V_D - V_S$$
$$= 10 - 2.35$$

**= 7.65V.** (1 mark)

Since  $V_G = 0V$

$$V_{GS} = V_G - V_S$$
$$= 0 - 2.35V$$

**= -2.35V** (1 mark)

**Question 4****POWER AMPLIFIER****[10 Marks]**

a. Used as the final stage of communication receivers or transmitters to provide signal power to speakers or transmitting antenna. (2 marks)

b.  $T = 1/200 \times 10^3$   
 $= 5\mu\text{S}$  (1 mark)

$$\begin{aligned} P_D(\text{avg}) &= (t_{\text{on}}/T)V_{\text{CE}}(\text{sat}) I_C(\text{sat}) \\ &= (1/5) \times 0.2 \times 100 \times 10^{-3} \\ &= \underline{\underline{4\text{mW}}} \end{aligned}$$
 (3 marks)

c. i) Heat sinks are made from aluminium with a matt black finish (1 mark)

ii) To remove excess heat from components so as to keep the internal temperature to a safe level. (1 mark)

iii) To create maximum surface area so that more heat can be dissipated. (2 marks)