



**COLLEGE OF ENGINEERING, SCIENCE & TECHNOLOGY (CEST)**

**SCHOOL OF ELECTRICAL & ELECTRONICS ENGINEERING**

**ELECTRICAL SERVICEMAN'S COURSE**

**EEE221- APPLIED ELECTRICITY 2**

**FINAL EXAMINATION – PENSTER 3, 2014**

**MARKING SCHEME GUIDE**

**EXAMINER: SANDEEP SARWAN LAL**

**BA CAMPUS**

**Section A**

**Multiple Choice**

**[10 Marks]**

1. D

2. D

3. B

4. B

5. C

6. A

7. C

8. A

9. B

10. B

**Section B**

**TRUE OR FALSE**

**[10 marks]**

1. F

2. F

3. F

4. T

5. F

6. T

7. T

8. T

9. F

10. F

**Section C**

**THEORY QUESTIONS**


**[80 Marks]**

**Question 1**

**3 PHASE SYSTEM**

**[20 Marks]**

**(2 marks)**

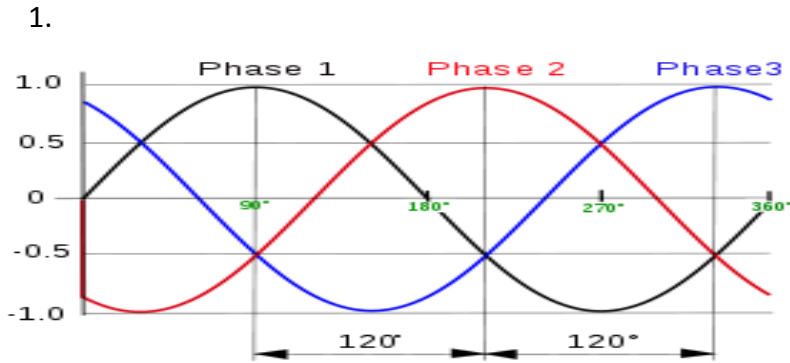


2. Red –White –Blue (RWB)

**(2 marks)**

3.

**Star**

**Delta**

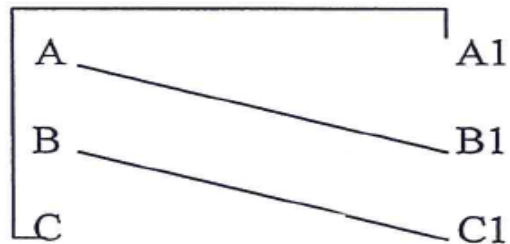

**(4marks)**

4.

Star system	Delta system
1. Similar ends connected	1. Dissimilar ends connected
2. For balanced loads and $I_L = I_p$ , $V_L = \sqrt{3} V_p$	2. For balanced loads and $V_L = V_p$ , $I_L = \sqrt{3} I_p$
3. Two voltage are available	3. One voltage available only
4. Line voltage leads phase voltage by $30^\circ$ E	4. Line current leads phase current by $30^\circ$ E
5. Suited for long distance power transmission	5. Suited to localized rotating machinery

(Any four)

**(4mark)**

5. a) Line voltage (1 mark)

$$\text{Line Voltage: } V_{line} = V_p \quad V_l = 415 \text{volts}$$

b) Phase voltage (1 mark)

$$\text{Phase Voltage: } V_p = 415 \text{volts}$$

c) Line current (1 mark)

$$\text{Line Current: } I_{line} = 3 \times I_p = 1.732 \times 5 = 8.66 \text{amperes}$$

d) Phase current: (1 mark)

$$\text{Phase Current: } I_p = \frac{I_{line}}{3} = \frac{8.66}{1.732} = 5 \text{amperes}$$

6. a) Line Current (2 marks)

Here impedance / phase  $Z_p = (10 + j 5) \Omega$   
 $= 11.18 \angle 26.57^\circ \Omega$   
 $E_L = 400 \text{ V}$   
 $E_p = E_L / \sqrt{3} = 400 / \sqrt{3} = 231 \angle 0^\circ \text{ V Ans.}$   
(a) In star, phase current = line current  
 $I_L = I_p = E_p / Z_p = 231 \angle 0^\circ / 11.18 \angle 26.57^\circ$   
 $= 20.65 \angle -26.57^\circ \text{ Amp}$

b) Power factor (2 marks)

(b) Power factor (P.F.)  $\cos \phi = \cos (-26.57^\circ) = 0.894 \text{ (lag)}$


**Question 2**

**THREE PHASE MOTOR**

**[20Marks]**

1. Squirrel-cage rotor and Wound rotor. (2 marks)

2.

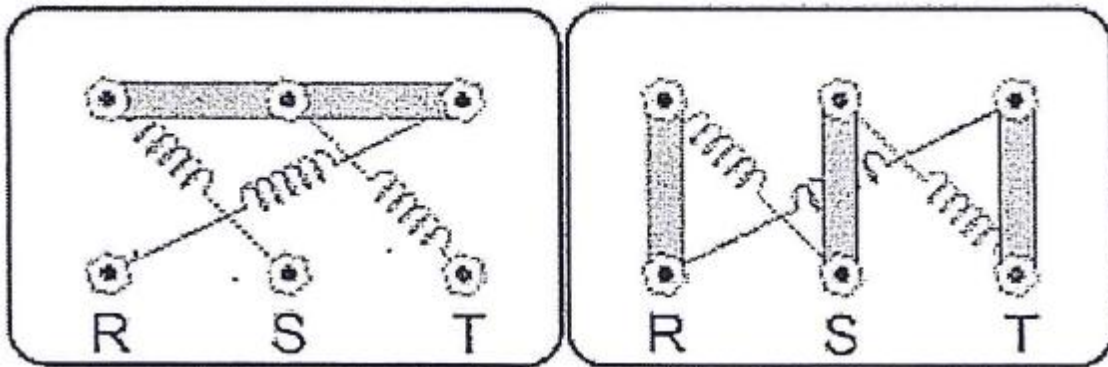

**(4 marks)**

3. Change the three phase sequence. (RWB to RBW or BWR or WRB or BRW or WBR)

**(2 marks)**

4.

- For the same power output, a three phase motor is physically smaller and lighter
- More efficient use of the iron core.
- Higher efficiency- less input power for the same input power
- For the same output power, line currents are smaller
- Suitable for power line frequencies in excess of several hundred hertz
- Less mechanical vibration, owing to magnetic fields of more constant strength
- Direction can be reversed externally by interchanging supply lines
- No starting mechanism or switches required

(Any Three).

**(3 marks)**

5.

a) Line voltage

(1 mark)

$$\text{Line voltage} = 415\text{volts}$$

b) Phase voltage

(1 mark)

$$\text{Phase voltage} = \frac{V_{\text{line}}}{3} = \frac{415}{1.732} = 240\text{volts}$$

c) Line current

(1 mark)

$$\text{Line current} = I_l = I_p \quad I_l = 3.6\text{amperes}$$


d) Phase current:

(1 mark)

$$\text{Phase current} = 3.6\text{amperes}$$

6.

(5marks)

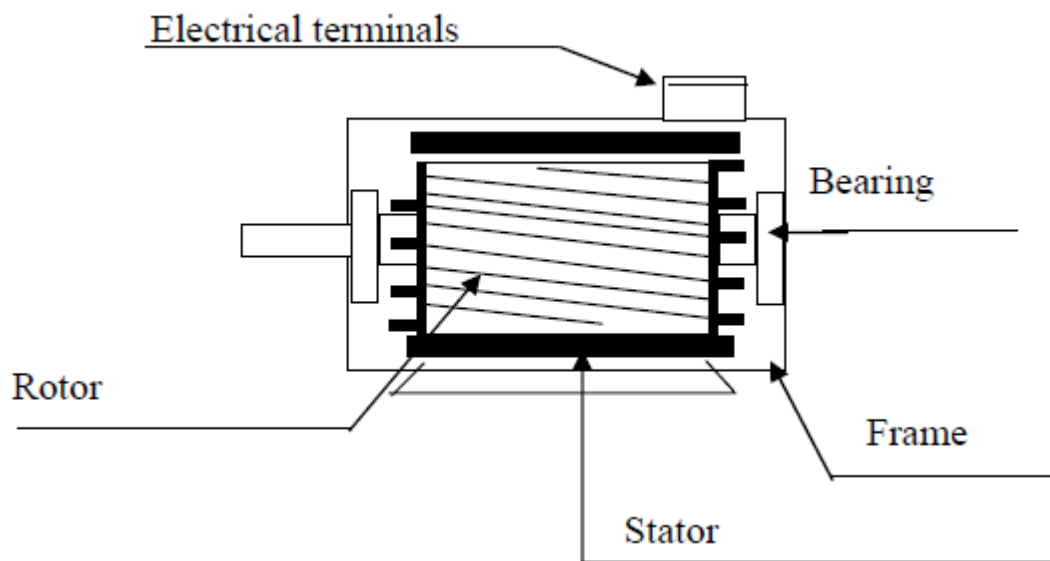

**Question 3**


**TRANSFORMERS**

**[20 Marks]**

- 1. i) Step up transformer
- ii) Step down transformer
- iii) Isolating transformer

**(3 marks)**

2.

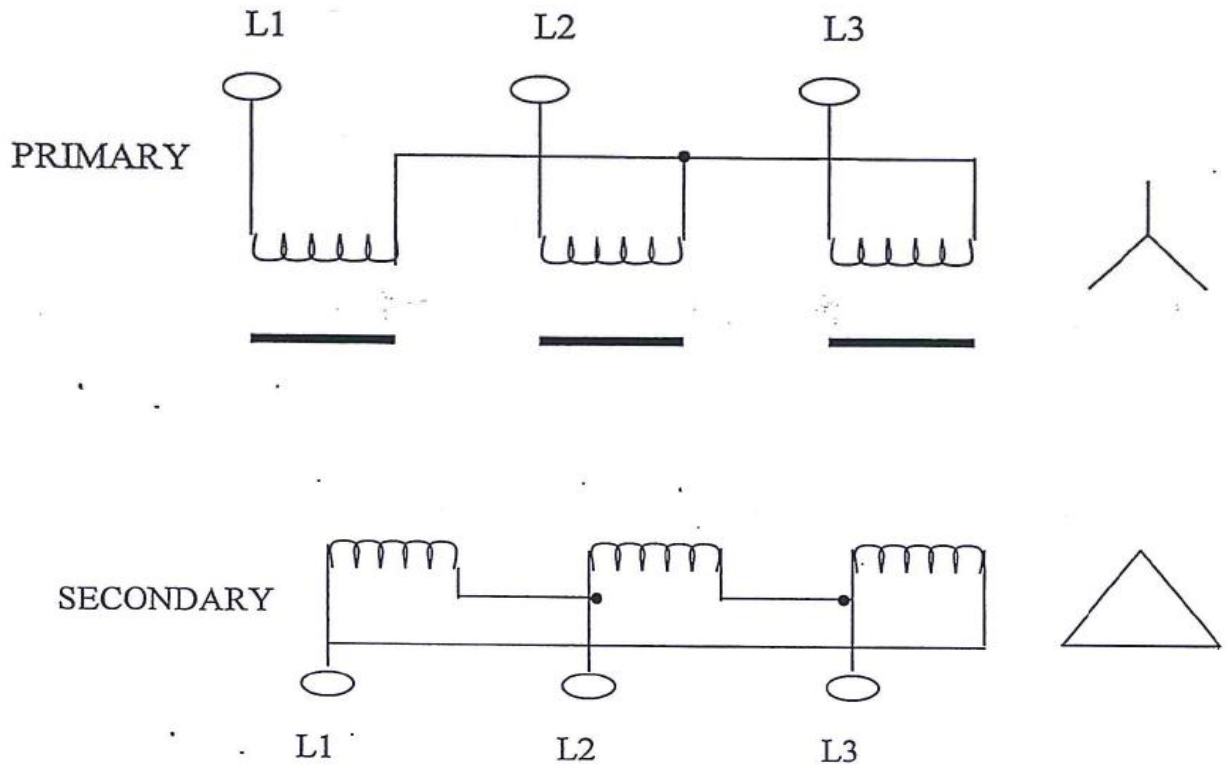

**(4 marks)**

3. a) 960:48

$$P1=960$$

$$P2 = 48$$

$$=20$$

Turn ratio = 20:1

**(2marks)**

b)  $V1 = 240V$

$$P1 = 960$$

$$P2 = 48$$

$$V2 = V1 \times N2/N1$$

$$= 240 \times 48/960$$

$$= \underline{12Volts}$$

**(2marks)**

5. Cooling is achieved by air in small transformers and oil in large transformers.

(4 marks)

6. Power supply

(1 mark)

7. i) Step down transformer

ii) Step up transformer

iii) Center tap transformer

iv) Isolation transformer


(4 marks)

**Question 4**

**RECTIFIERS**


**[20 Marks]**

1.a) Single phase half wave

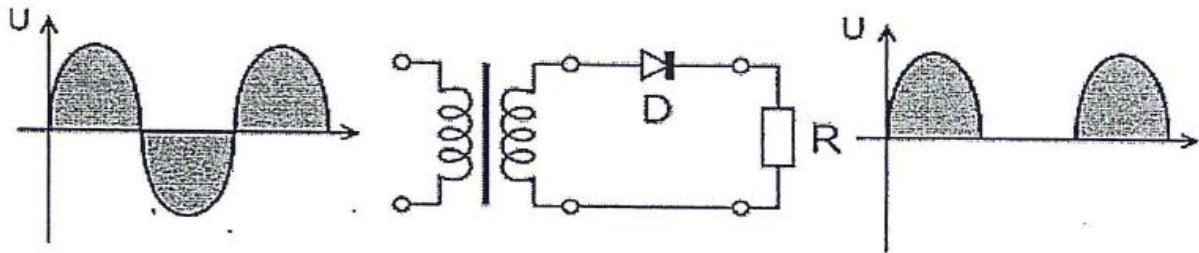

(3 marks)


a) Single phase bridge

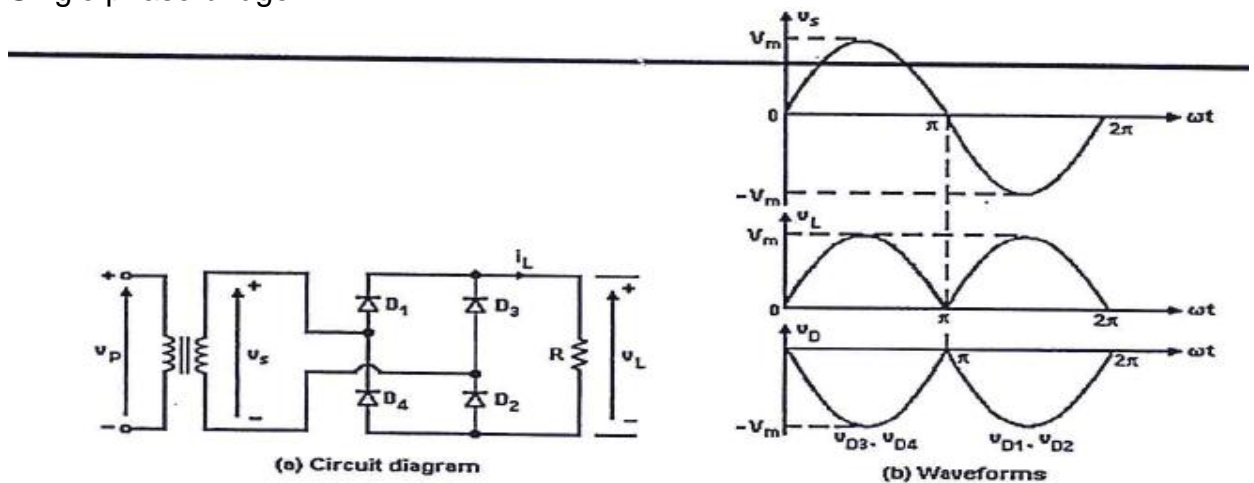

(3 marks)



b) Three phase full wave bridge

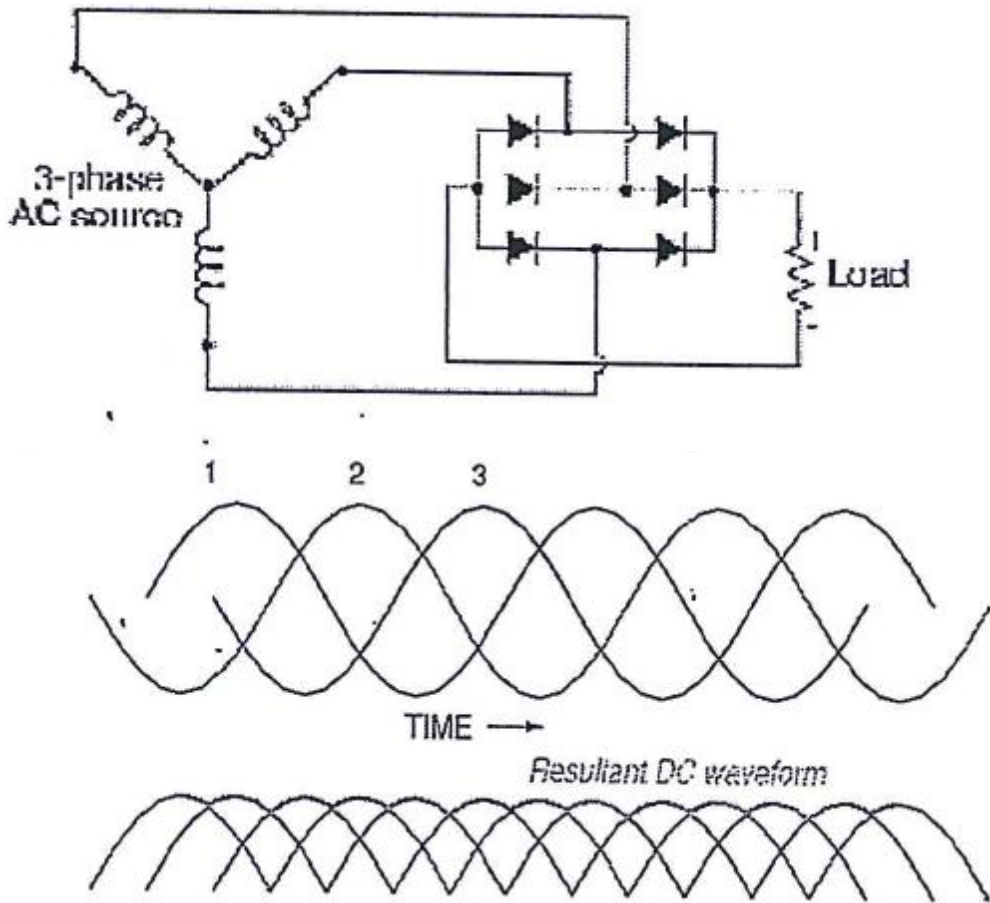

(3 marks)

2.

$$V_{d.c.} = 0.45V_S = 0.45 \times 240 = 108v$$

$$I_{d.c.} = \frac{V_{d.c.}}{R} = \frac{108}{100} = 1.08amps$$

$$Power = I^2 R = 1.08^2 \times 100 = 116watts$$

(4 marks)

2. a) The load voltage

$$V_L = 0.9V_{a.c.} = 0.9 \times 32 = V_L = 28.8V$$

(1mark)

b)The load current

$$I_L = \frac{V_L}{R_L} = \frac{28.8}{5.0} = I_L = 5.76A$$

(1 mark)

c) the ripple voltage

$$V_R = \sqrt{2}V_{a.c.} = \sqrt{2} \times 32 = V_R = 42.25V$$

(2 marks)

d)The ripple frequency

$$f_R = 2f_{supply} = 2 \times 50 = f_R = 100Hz$$

(1mark)

e) The peak root value

$$PRV = 2\sqrt{2}V_{a.c.} = 2 \times \sqrt{2} \times 32 = PRV = 90.5V$$

(2 marks)

THE END