

Answer all Questions


Question 1

State the following:

- a) Thevenin's Theorem. (1.5marks)
- b) Norton's Theorem. (1.5marks)
- c) Maximum power transfer theorem. (2marks)


Question 2

Reduce the circuit shown to its Thevenin and Norton equivalent circuits.

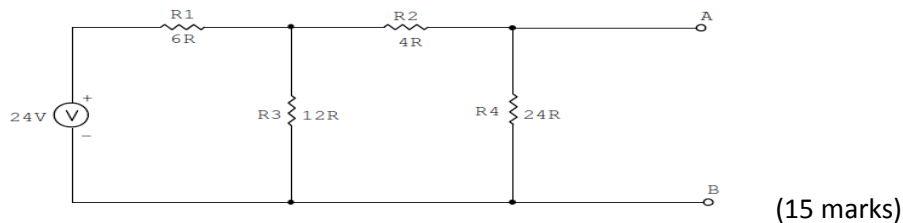


Question 3

For the circuit shown in Fig. 1, find the value of R_L for maximum power transfer. What will be the value of maximum power?

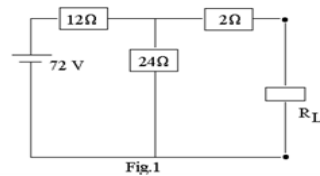

Question 4

Calculate the voltage applied across the circuit given below if, at a frequency of 2000Hz, 2V are dropped across the 1000 ohms resistance. (10 marks)

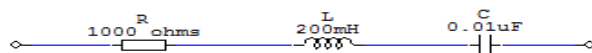


Question 5

A balanced Y-connected load with a phase resistance of 40 ohms and a reactance of 25 ohms is supplied by a balanced, positive sequence Δ- connected source with a line voltage of 210 V. Calculate the phase currents. Use V_{ab} as reference.

(10marks)

Question 6

Execute $Y \rightarrow \Delta$ (Rab)

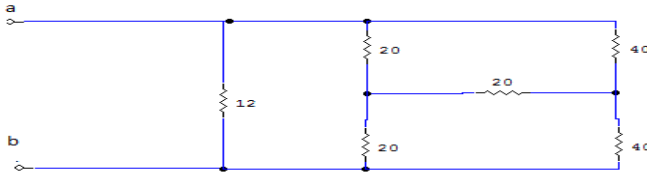

(10 marks)


Question 7

Explain the purpose of the transformers in power distribution with aid of diagrams

(10marks)

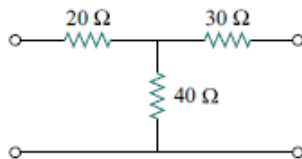Question 8

Determine the z parameters for the circuit below



(10 marks)

Question 9

Determine the phase sequence of the set of voltages.

(10 marks)

$$V_{an} = 200 \cos(\omega t + 10^\circ)$$

$$V_{bn} = 200 \cos(\omega t - 230^\circ)$$

$$V_{cn} = 200 \cos(\omega t - 110^\circ)$$

Question 10

Determine the Laplace Transform of each of the following functions.

a) $u(t)$ (3marks)

b) $e^{-at} u(t)$ (3marks)

c) $\delta(t)$ (4marks)

-----THE END-----