



**FIJI NATIONAL UNIVERSITY**

**COLLEGE OF ENGINEERING, SCIENCE & TECHNOLOGY**  
**SCHOOL OF ELECTRICAL & ELECTRONIC**

**ENGINEERING**

**TRADE DIPLOMA IN ELECTRICAL ENGINEERING**  
**STAGE 5**

**EEE571—ELECTRICAL POWER NETWORKS & THEOREMS**

**TRIMESTER 3 - 2015.**

**Total marks-100%-----Duration: 2Hrs 10 Minutes**

**DAY/DATE: \_\_\_\_\_ TIME: \_\_\_\_\_ ROOM: As per timetable.**


**INSTRUCTIONS TO STUDENTS**

1. *You are allowed 10 minutes Extra reading time during which you are NOT to write.*
2. *Begin each answer on a fresh page and use both sides of the sheet.*
3. *Write your candidate-number at the top of each attached sheet.*
4. *Insert all written sheets in their correct sequence and secure with string.*
5. *For all sheets of paper on which rough/draft work has been done, cross it though and you MUST ATTACH to your answer scripts.*
6. *Write clearly the number(s) of the question(s) attempted on the top of each sheet.*
7. *Answer all Questions*
8. *Show all workings where necessary.*
9. *Do not use programmable calculators, especially the ones that does the conversions of number systems.*
10. ***CHECK YOUR WORK BEFORE YOU LEAVE THE ROOM!***

Attempt all the questions


**Question 1**

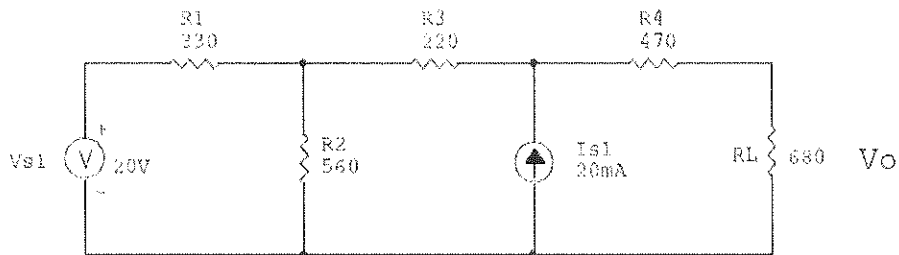a) Reduce the circuit shown to its Thevenin and Norton equivalent circuits.



(15 marks)

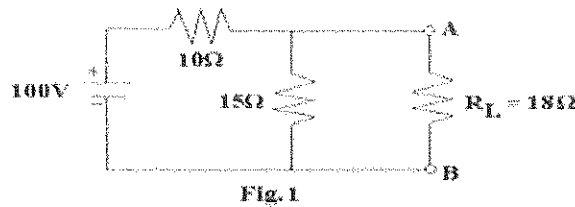
b) For the circuit shown in Fig. 2 find the current in the load resistance  $R_L = 18\Omega$  and the voltage across it by Norton's theorem and verify the result by applying Thevenin's theorem.



(5marks)

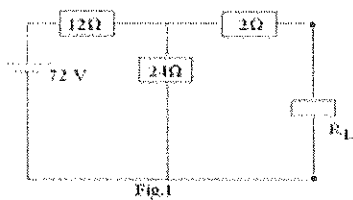**Question 2**


For the circuit shown in Fig. 1, find the value of  $R_L$  for maximum power transfer. What will be the value of maximum power?



(5 marks)

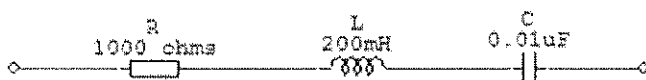**Question 3**


Calculate the voltage applied across the circuit given below if, at a frequency of 2000Hz, 2V are dropped across the 1000 ohms resistance.



(5 marks)

Question 4


Execute  $Y \rightarrow \Delta (R_{ab})$

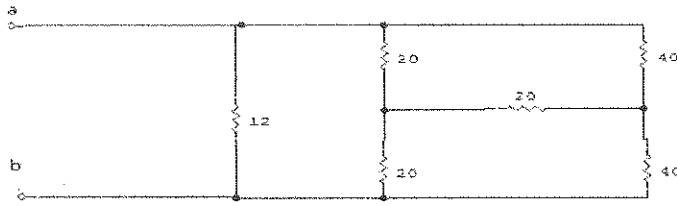

(10 marks)

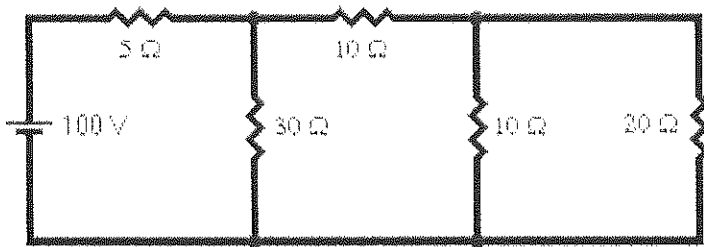Question 5

Use nodal analysis to find the voltage at each node of this circuit.




(10 marks)

Question 6


a) Given the following circuit. Determine the Z parameters

(8 marks)

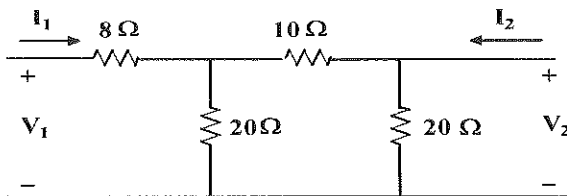

b) We modify the network as shown by adding elements outside the two ports

(12 marks)

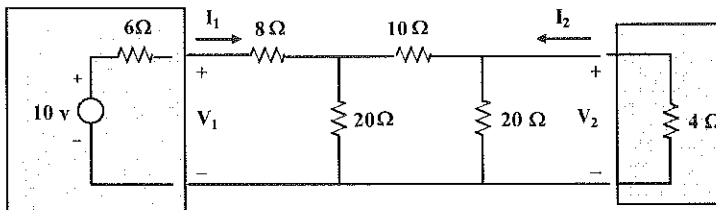

Find the values for  $V_1$ ,  $V_2$ ,  $I_1$  and  $I_2$

Question 7

Determine the phase sequence of the set of voltages.

$$V_{an} = 200 \cos(\omega t + 10^\circ)$$

$$V_{bn} = 200 \cos(\omega t - 230^\circ)$$

$$V_{cn} = 200 \cos(\omega t - 110^\circ)$$

(10marks)

Question 8

Determine the Laplace Transform of each of the following functions.

a)  $t^2 - 2t$

(3marks)

b)  $(t^2 - 3)^2$

(3 marks)

c)  $\cos 2\pi t$

(4 marks)

Question 9

A balanced Y-connected load with a phase resistance of 40 ohms and a reactance of 25 ohms is supplied by a balanced, positive sequence  $\Delta$ - connected source with a line voltage of 210 V. Calculate the phase currents. Use  $V_{ab}$  as reference.

(10marks)

-----THE END-----