



COLLEGE OF ENGINEERING, SCIENCE & TECHNOLOGY (CEST)

SCHOOL OF ELECTRICAL & ELECTRONICS ENGINEERING

CERTIFICATE IV IN ELECTRICAL ENGINEERING-STAGE 4

EEE448- ELECTRONICS FOR ELECTRICIANS 2

FINAL EXAMINATION – PENSTER 1, 2016

DAY/DATE: as per timetable. TIME: 2 HOURS 10 MINUTES

ROOM: as per timetable.

**INSTRUCTIONS TO STUDENTS**

1. *You are allowed 10 minutes Extra reading time during which you are NOT to write.*
2. *Begin each Son a fresh page and use both sides of the sheet.*
3. *Write your candidate-number at the top of each attached sheet.*
4. *Insert all written foolscaps, graph paper, drawing paper, etc. in their correct sequence and secure with string.*
5. *For all sheets of paper on which rough/draft work has been done, cross it though and you MUST ATTACH to your answer scripts.*
6. *Write clearly the number(s) of the question(s) attempted on the top of each sheet.*
7. **ANSWER ALL QUESTIONS.**
8. *Show all workings where necessary.*
9. *Do not use programmable calculators, especially the ones that does the conversions of number systems.*
10. **ALWAYS CHECK YOUR WORK BEFORE YOU LEAVE THE ROOM!**

**Section A****Multiple Choice****[30 marks]**

Select the best answer from the options given by circling the letter (A, B, C or D) in the matrix supplied at the end of the Question Paper and attach to your Answer Booklet.

1. An ideal operational amplifier has
  - a) infinite output impedance
  - b) zero input impedance
  - c) infinite bandwidth
  - d) All of the above
  
2. How many diodes are found in full – wave bridge single phase rectification?
  - a) 2
  - b) 4
  - c) 1
  - d) 8
  
3. If the supply frequency of a single phase is 50 hertz, the ripple frequency of a full-wave rectifier is:
  - a) 100 Hz.
  - b) 12.5 Hz.
  - c) 25 Hz.
  - d) 50 Hz.
  
4. What is the output voltage of the fixed regulator type?  
7924
  - a) -792 V
  - b) +82 V
  - c) +24 V
  - d) -24 V
  
5. The ratio between differential gain and common-mode gain is called:
  - a) Amplitude
  - b) differential-mode rejection
  - c) common-mode rejection
  - d) phase

6. What is the first procedure when troubleshooting any equipment?

- a) Signal injection.
- b) Visual check.
- c) Powering the equipment on.
- d) Visualising the waveform by using a CRO.

7. Name the part of the cathode ray oscilloscope where the beam of electrons is first seen.

- a) Grids.
- b) Deflection plates.
- c) Filament.
- d) Faceplate.

8. Troubleshooting a digital circuit by means of a \_\_\_\_\_ is the most reliable test instrument to use to measure the voltage.

- a) Logic probe.
- b) CRO.
- c) DMM.
- d) Signal generator.

9. Which of the following pin numbers represent the output terminal of LM741 operational amplifier?

- a) 2
- b) 3
- c) 4
- d) 6

10. Single – phase bridge rectifier normally uses:

- a) Two diodes in it's operation.
- b) One diode in it's operation.
- c) Four diodes in it's operation.
- d) None of the above.

11. VCE approximately equals \_\_\_\_\_ when a transistor switch is cut off.
- a) VCC
  - b) VB
  - c) 0.2V
  - d) 0.7V
12. Identify the term that describes the value of the waveform that will produce the same heating effect whether if the system is DC or AC.
- a) Maximum value.
  - b) Average value.
  - c) Root mean square value.
  - d) Peak value.
13. Name the device used to convert AC to DC:
- a) Inverter.
  - b) Rectifier.
  - c) Converter.
  - d) Filter.
14. During troubleshooting, the appropriate test instrument; \_\_\_\_\_ is used for signal injection.
- a) CRO
  - b) Signal Generator
  - c) DMM
  - d) Both a) and b)
15. Which type of filters is used in DC power supplies?
- a) High pass filters.
  - b) Band – pass filters.
  - c) Band – stop filters
  - d) Low pass filters
16. Which test instrument is used to measure the precise resistance of a 100  $\Omega$  resistor?
- a) CRO.
  - b) Voltmeter.
  - c) Ohmmeter.
  - d) Ammeter.

17. Unregulated DC power supplies normally have:

- a) No regulator connected after the rectifier stage.
- b) No regulator connected after the filter stage.
- c) A regulator connected after the filter stage.
- d) A regulator connected before the filter stage.

18. Another name for an astable timer is:

- a) Free running
- b) One shot
- c) Disruptive running
- d) No running

19. The output of a NOT gate is high when

- a) The input is LOW
- b) The input is HIGH
- c) The input changes from LOW to HIGH
- d) Voltage is removed from the gate.

20. Which two components are commonly used in light dimmers?

- a) SCR and Diac
- b) SCR and Triac
- c) Triac and Diac
- d) MOSFET and Diac

21. To operate properly, a transistor's base-emitter junction must be forward biased with reverse bias applied to which junction?

- a) collector-emitter
- b) base-collector
- c) base-emitter
- d) collector-base


22. A transistor has a  $\beta_{dc}$  of 250 and a base current,  $I_B$ , of 20  $\mu\text{A}$ . The collector current,  $I_C$ , equals:

- a) 500  $\mu\text{A}$
- b) 5 mA
- c) 50 mA
- d) 5 A

23. Name the component used to emit light and is used as an indicator

- a) Diode
- b) Photo diode
- c) Photo transistor
- d) LED

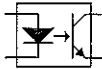24. Name the component used to interface two circuits of different current magnitudes.



- a) LED
- b) Photo transistor
- c) LED and photo transistor
- d) Opto-coupler

25. The output of an AND gate is LOW

- a) All the time
- b) When any input is LOW
- c) When any input is HIGH
- d) When all inputs are HIGH

26. Identify the transformer used to change the voltage from 240Vac to 12 Vac.

- a) Matching transformer
- b) Step-down transformer
- c) Step-up transformer
- d) Isolation transformer

27. Name the best test instrument to measure frequency.

- a) DMM
- b) Frequency counter
- c) CRO
- d) All of the above

28. The Boolean expression  $Y = \overline{A}B$  is logically equivalent to what single gate?

- a) NAND
- b) NOR
- c) AND
- d) OR






29. If you have to measure current, which selection will you choose?


- a) Ammeter
- b) Ohmmeter
- c) Voltmeter
- d) Capacitance meter.

30. Choose the best test instrument that has a multi – selection applications for measuring any quantity instead of having more than one test instrument.


- a) CRO
- b) Multimeter
- c) Ammeter
- d) Ohmmeter

**SECTION B: Matching [30marks]**

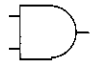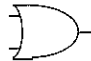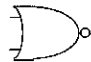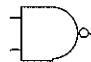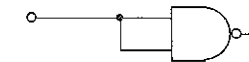1	Block diagram	A	
2	LM317	B	
3	Step up transformer	C	
4	Circuit Diagram	D	
5	LM555	E	
6	Component layout diagram	F	Illustrates the exploded views of an equipment
7	Soldering	G	12 Vac to 240 Vac

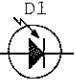8	Step down transformer	H	+ve adjustable regulator
9	NAND gate	I	Components used to interface a high current circuit to a low current circuit
10	LM741	J	Shows a design in a logical fashion that contains component symbols
11	Analogue multimeter	K	-5V
12	Inverting amplifier	L	Instrument that visualizes any waveform
13	AND gate	M	Removing of solder
14	Dual DC power supply unit	N	240 Vac to 12 Vac
15	Photo diode	O	+ 12 V
16	Desoldering	P	In phase
17	Focus Knob	Q	+ve and -ve voltages
18	NOR gate	R	Bonding of two metals
19	Light emitting diode	S	
20	7812	T	180° out of phase
21	Make trace to increase or decrease in amplitude	U	Time/division knob
22	NOT gate	V	OP-Amp
23	AC, GND, DC	W	Input switch
24	Make trace to increase or decrease in time period	X	Timer IC
25	Non-inverting amplifier	Y	Shows the stages of any equipment by the indications of arrows
26	Cathode Ray Oscilloscope	Z	Volts/division knob
27	OR gate	AA	Part of the CRO that functions as a trace clarity knob



28	Opto-couplers	AB	D2 
29	7905	AC	Abbreviated as VOM
30	Assembly Diagram	AD	Shows the physical sizes of the components onto a PCB

**SECTION C: Definitions, Statements of Facts, & Formulas**

**[10 marks]**

1. Briefly define the following terms as they refer to semiconductors:

a) Doping

(1mark)

b) Holes

(1mark)

2. The Cathode Ray Oscilloscope (CRO) has several applications. Name any 4 of them.

(4 marks)

3. Fill in the blank spaces.

Name of the Test Equipments	Function	Operating Parameters (Voltage / Current)	Application of such Test Meters/Equipments
Series Test Lamp			
Clamp meter			
Neon Test Lamp (Screwdriver)			
Logic Probes			


(4 marks)

**Section D**

**Sketches, Analysis & Operation**

**[30 Marks]**

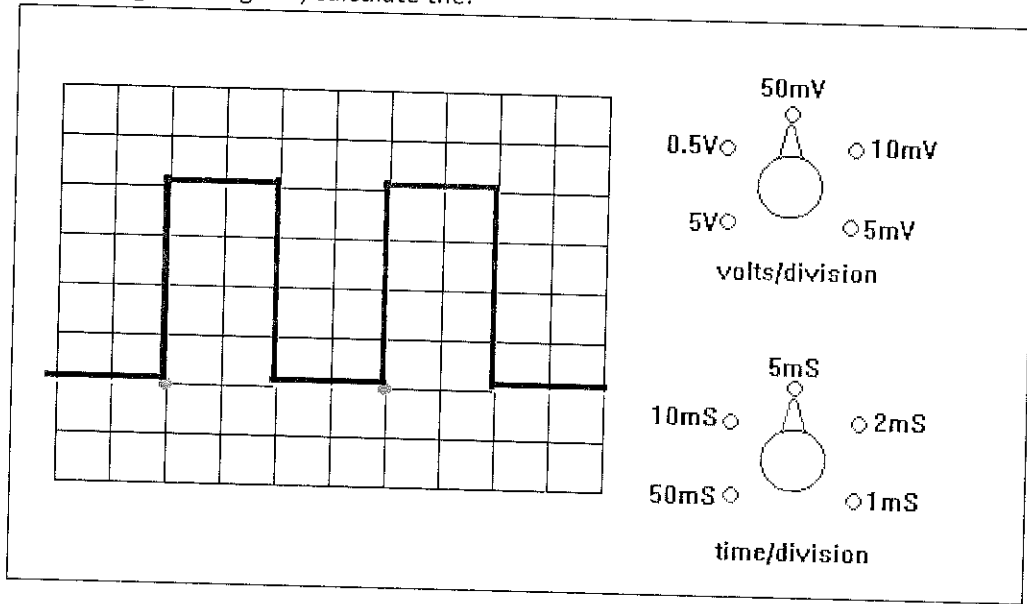1. From the given diagram, calculate the:



a) Frequency. (2marks)


b) Amplitude. (2 marks)

2. List three (3) comparison of Digital and Analogue meters (3 marks)

3. With the use of suitable sketches clearly describe the operation of a Full-Wave Bridge Rectifier circuit.


(Marks: Cct-2, Waveforms-2, Operation-2) (6 marks)

4. A certain circuit is given:

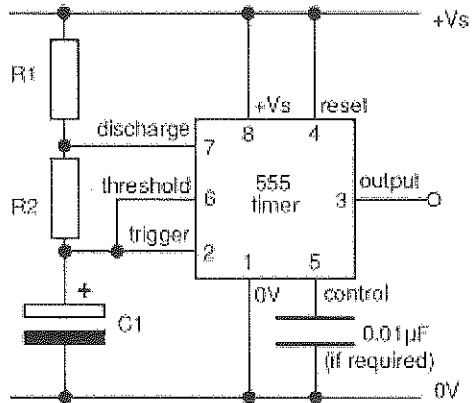


- Identify the application. (1 mark)
- Sketch the waveforms at Pins 2 and 3. Showing them on a common vertical axis. (2 marks)
- What is the frequency of the O/P signal if  $R1 = 1 \text{ k}\Omega$ ,  $R2 = 10 \text{ k}\Omega$  and  $C1 = 0.1 \text{ }\mu\text{F}$ ? (3 marks)

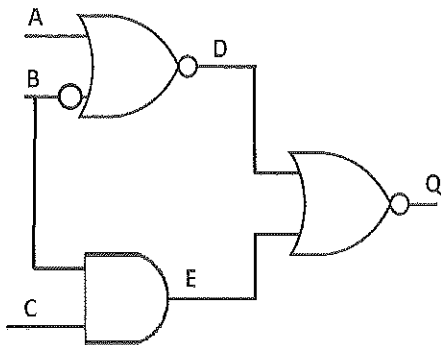5. Determine the output (Q) combination of the circuit given below. (5marks)



Inputs			Outputs		
A	B	C	D	E	Q
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

6. An SCR can be represented as shown:

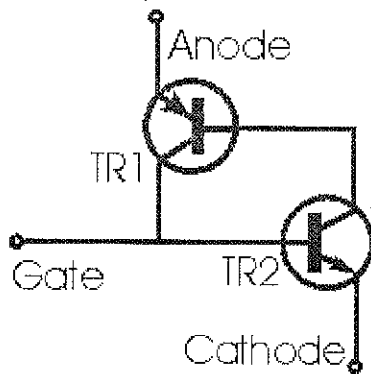

- a) State the voltage polarities at the Anode & Cathode. (2 marks)
- b) What happens when a +ve pulse of current is applied to the Gate? (2 marks)
- 7.i) State the purpose of a filter in a DC power supply. (1 mark)
- ii) Sketch a basic LED voltage indicator, showing typical voltages and currents. (2 marks)

THE END



EQP RECEIPT CHECKLIST FORM

Particulars	Details/Comments (To be filled by Unit Lecturer)	Tick if present on EQP (To be filled by exams staff)
<b>Cover Page</b>		
Fiji National University with Logo	✓	
College	✓	
School	✓	
Program	✓	
Unit Code	✓	
Unit Name	✓	
Examination Period	✓	
Duration of Examination	✓	
Instructions	✓	
Total Number of Pages	✓	
<b>Other Pages</b>		
Footer	Page Number	✓
	Unit Code	✓
	Examination Period	✓
<b>Last Page</b>		
The End	✓	
<b>Overall</b>		
Proper Print	✓	
Examination Requirements (FNU/E-1)	✓	
Moderator's Report (FNU/E-3)	✓	
ERRS (Class List)	✓	
Unit Coordinator/Principal Lecturer's Name	✓	

DISPATCHED BY (SCHOOL REP)

NAME: AKLESH KUMAR

SIGN: [Signature]

DATE: 19/02/2016

RECEIVED BY (EXAMS REP)

NAME: \_\_\_\_\_

SIGN: \_\_\_\_\_

DATE: \_\_\_\_\_





Class Listing

School of Electrical & Electronics Engineering

Ba campus

Penster1

2016

EEE448 Electronics for Electricians 2 NL

StudentID	Name	Status	Mon	Sponsor	Outstanding Fee
-----------	------	--------	-----	---------	-----------------

Certificate IV in Electrical Engineering 0

2011001720	Elvish Richelle Chand	EA			
2012010335	Izaz Azizz Ali	EA		- Full	
2013114616	Kavinesh Kartik Pillay	EA		- Full	
2013117599	Krishan Kamit Reddy	EA			
2012010863	Mohammed Shahil	EA			
2013113125	Mohammed Shahir	EA		- Full	
2007004827	Muni Krishn Chandiran	EA		- Full	
2013117399	Sahil Shafran Ali	EA			

		8			<b>Total Owing: 0.00</b>
<b>Total Count:</b>		8			<b>Grand Total: 0.00</b>

