

Section – A:**[20 marks]****Multiple Choice****(12 marks)**

In this section, read the question properly/ carefully and select your best answer by writing the alphabet of your choice along the question number in the answer sheet.

(1 mark each)

1. The value of natural logarithm e is approximately?
 - (a) 2.718
 - (b) 2.728
 - (c) 3.142.
 - (d) 2.782.

2. In RC Timing circuits, during the 1st time constant, the capacitor is charged to about --- of the source voltage.
 - (a) 62.3%
 - (b) 63.2%
 - (c) 62.4%.
 - (d) 62.7%.


3. What is the *frequency* component of the following voltage equation,
 $v = 12 \sin 377t + 70^\circ$.
 - (a) 497
 - (b) 70
 - (c) 377
 - (d) 377+70

4. What is the *phase shift* component of the following voltage equation,
 $v = 12 \sin 377t + 70^\circ$.
 - (a) 377t + 70
 - (b) 70
 - (c) 377
 - (d) 12

5. Determine what *frequency* will an inductor of 5mH will have the same reactance with a capacitor of 0.1uF?
 - (a) 712kHz
 - (b) 7.21kHz
 - (c) 7.12kHz
 - (d) 721kHz.


6. In a RCL series circuit, a 240v supply with 50 Hz connected with a resistor of 20Ω , capacitor of $80\mu\text{F}$ and inductor of 0.25H . Determine the inductive reactance?
- (a) $785.3\text{k}\Omega$
 (b) 785.3Ω
 (c) $78.53\text{k}\Omega$
 (d) 78.53Ω .
7. In a RCL series circuit, a 240v supply with 50 Hz connected with a resistor of 20Ω , capacitor of $80\mu\text{F}$ and inductor of 0.25H . Find the capacitive reactance?
- (a) 39.79Ω
 (b) $39.79\text{k}\Omega$
 (c) $39.79\text{M}\Omega$
 (d) 39.97Ω .
8. In a RCL series circuit, a 240v supply with 50 Hz connected with a resistor of 10Ω , capacitor of $60\mu\text{F}$ and inductor of 0.20H . The impedance of the circuit will be:-?
- (a) 42.60Ω
 (b) 13.93Ω
 (c) $43.6\text{k}\Omega$
 (d) $42.60\text{k}\Omega$.
9. Convert the following voltage $v_a = 50 \sin(377t + 30^\circ)$ from time domain into phasor domain and re-write the voltage into phasor format.
- (a) $v_a = 70.71\text{v} \angle 30^\circ$
 (b) $v_a = 35.35\text{v} \angle 21^\circ$
 (c) $v_a = 70.71\text{v} \angle 21^\circ$
 (d) $v_a = 35.35\text{v} \angle 30^\circ$.
10. Which of the following dependent sources is not appropriate?
- (a) voltage controlled voltage source
 (b) current controlled voltage source
 (c) voltage controlled current source
 (d) current controlled current source

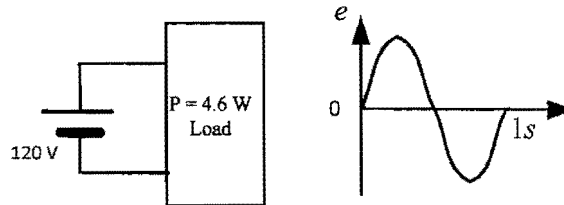11. A system of 120V dc delivers 4.6W to the load as per diagram below. Find the peak value of the applied voltage (E_m) and the current (I_m) if the source to delivered same power to the same load.



- (a) $E_m = 149.24v, I_m = 42.54mA$
 (b) $E_m = 159.86v, I_m = 42.42mA$
 (c) $E_m = 84.85v, I_m = 54.21mA$
 (d) $E_m = 169.71v, I_m = 54.21mA$

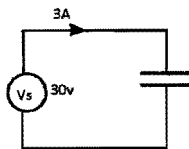12. In a purely capacitive circuit, current (i) leads voltage (v) by 90° , determine the average power in the capacitor.



- (a) $P_{av} = 0w$
 (b) $P_{av} = 45w$
 (c) $P_{av} = 100w$
 (d) $P_{av} = 1Kw$

Short Answer

(8 marks)

In this section, read the question properly/ carefully and determine your answer correctly by writing it in the answer sheet provided.

1. The voltage across a $5.6\mu\text{F}$ Capacitor is given as $v = 35 \sin 300t$. What is the sinusoidal expression for the current? [2 marks]


2. Name 2 types of dependent power sources. [2 marks]

3. Determine the average power delivered to networks having the following input voltage and current as described below: - [2 marks]

$$v = 120 \sin(\omega t - 60^\circ)$$

$$i = 20 \sin(\omega t - 45^\circ)$$

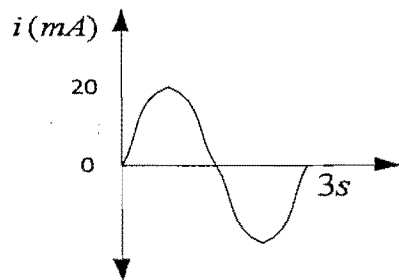4. Find the Effective Values(RMS) of the sinusoidal waveform in graph below:- [2 marks]




Section – B: - Answer all question in this section


[50 marks]

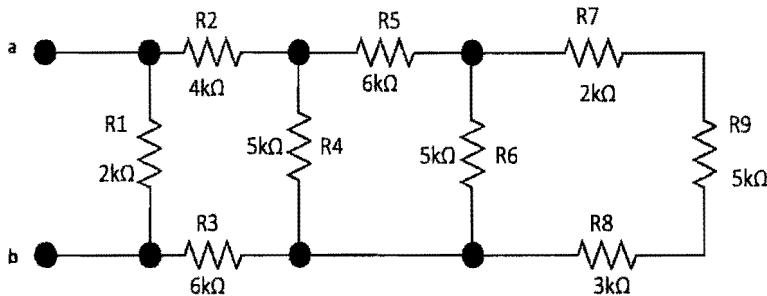Question 1 - Series/Parallel Resistor Network


- (a). A resistive circuit is given below. Workout the R_{eq} between terminal a and b. (4 marks)



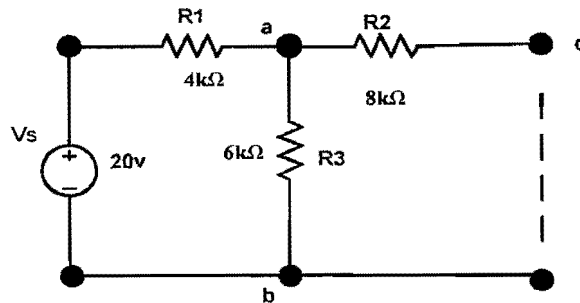- (b). For the Series/Parallel Resistive network circuit below, find the following:-




- i) The voltage across each resistor. (4marks)
 - ii) The current through the circuit. (1mark)
 - iii) If there is a short between points c-b, work out the current through the parallel branch (3marks)
 - iv) The current through the circuit if points a-b is shorted. (2marks)
- (c). Find the current flowing through each branch of the circuit in figure below.... (6 marks)

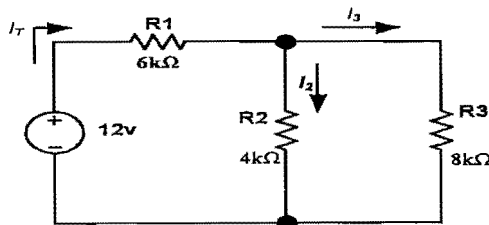


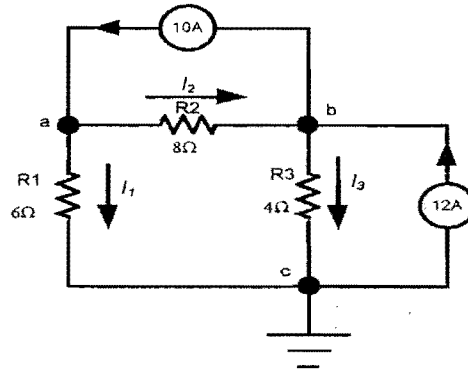Question 2 - Nodal Analysis

(a). Using Nodal Analysis method, find the voltage at node "a" & node "b" in a circuit given below. (10 marks)




(b). Find the current in each resistor in the circuit below. (10 marks)

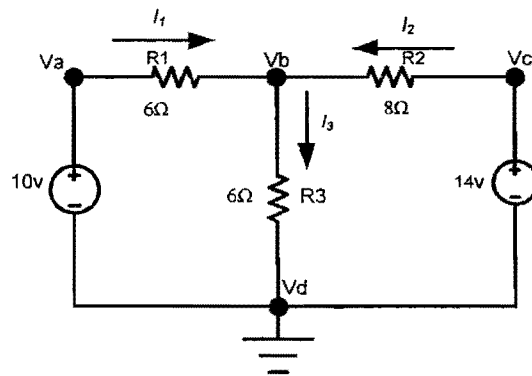

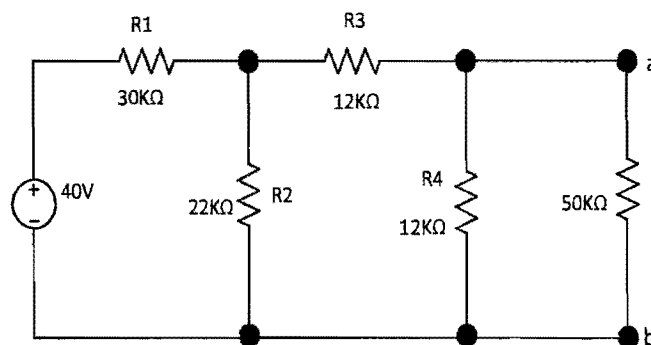Question 3 - Thévenin's Theorem

From the circuit given below, determine Thévenin's equivalent circuit and calculate the current through the load resistor. (10 marks)



Section – C:


[30 marks]

Select any **THREE (3)** questions from the seven(7) question given below.

Question 1

Use complex algebra [j-notation] application to:-

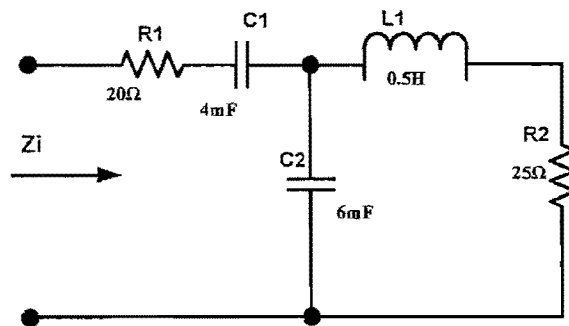
- i. Determine the input impedance of the circuit shown below. [7 marks]
- ii. Plot its phasor diagram [3 marks]



(use $\omega = 10 \text{ rad/s}$)


Question 2

For the circuit below, show the full calculation of the Gain = $I_O(\omega) / I_I(\omega)$ and determine the poles and zeroes of the circuit below using the RL and RC responses. (10 marks)

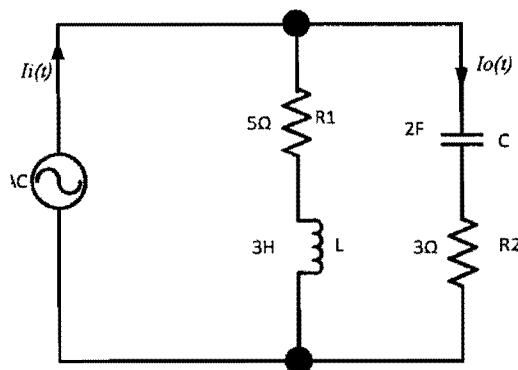

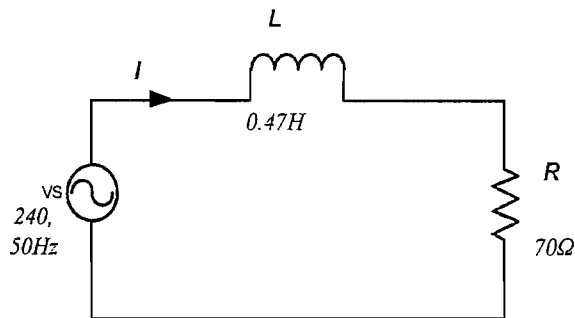Question 3.


- (a). Determine the impedance and its phase angle of the RL circuit below?
(6 marks)



- (b). The voltage across a $3\mu\text{F}$ Capacitor is given as $v = 30 \sin 377t$. What is the sinusoidal expression for the current and Sketch the voltage and current curves.
(4 marks)

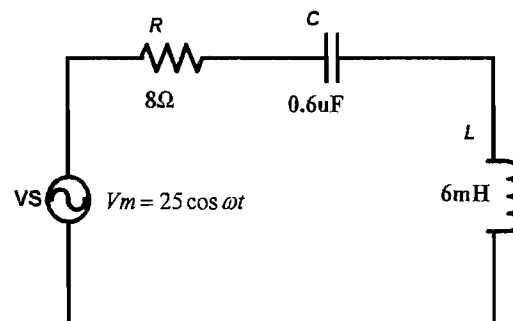Question 4

For the RLC circuit below, resistor = 8Ω , capacitor = $0.6\mu\text{F}$ and inductor = 6mH , show all the necessary calculation to determine the following:-
(10 marks)




(use $\pi = 3.14$)

- a) The resonant frequency (2 marks)
b) Half power frequencies (4 marks)
c) Quality Factor (2 marks)
d) Bandwidth (2 marks)


Question 5

For the circuit shown below, calculate and determine the Norton's equivalent circuit. (10 marks)

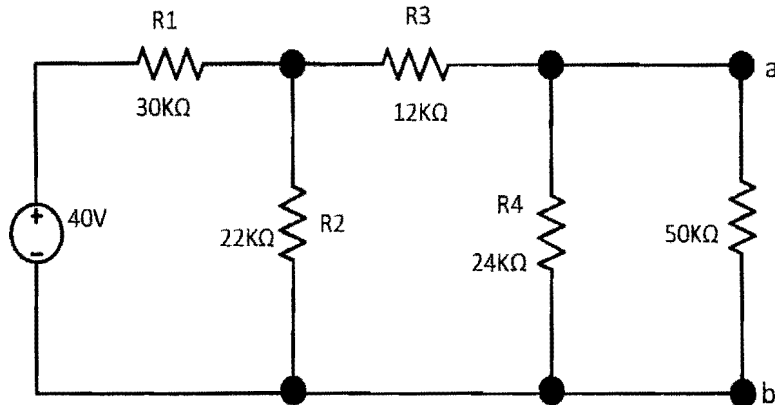

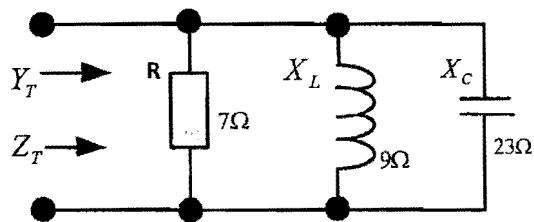Question 6


For the parallel RCL network below. (10 marks)



- Find the admittance of each parallel circuit. (3 marks)
- Determine the input admittance. (2 marks)
- Calculate the input impedance (2 marks)
- Draw the input impedance diagram. (1½ marks)
- Draw the admittance diagram. (1½ marks)

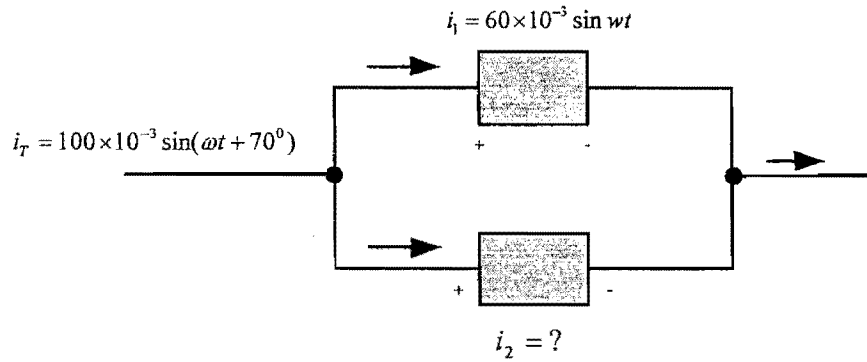Question 7

Determine the current i_2 for the network in the circuit below. (10 marks)



----- END OF PAPER -----

Appendix 1

Formulas

$$1. \quad w_x = R/2L + \sqrt{(R/2L)^2 + 1/LC}$$

$$2. \quad w_y = -R/2L + \sqrt{(R/2L)^2 + 1/LC}$$

$$3. \quad f_0 = 1/2\pi\sqrt{LC}$$

$$4. \quad Q = \frac{1}{w_0 CR}$$

$$5. \quad B = w_0^2 CR$$

$$6. \quad X_L = 2\pi fL$$

$$7. \quad X_C = \frac{1}{2\pi fC}$$

$$9. \quad I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2, \quad \beta_1 [(V_{DD} - 2V_T)V_{ON} - 0.5^2 V_{ON}^2]$$

$$10. \quad f_H = \pm \frac{8f_0}{V_C}, \quad V_{DS} = V_{DD} - I_D R_D$$