



**COLLEGE OF ENGINEERING, SCIENCE & TECHNOLOGY (CEST)**

**SCHOOL OF ELECTRICAL & ELECTRONICS ENGINEERING**

**CERTIFICATE III IN ELECTRONIC ENGINEERING**

**CERTIFICATE IV IN ELECTRONIC ENGINEERING**

**EEC309- DIGITAL ELECTRONICS I**

**FINAL EXAMINATION – QUARTER 2, 2019**

**DATE:** As per timetable

**TIME:** As per timetable

**TIME ALLOWED:** 2 HOURS 10 MINUTES

### **INSTRUCTIONS TO STUDENTS**

- 1. You are allowed 10 minutes extra reading time during which you are NOT to write.*
- 2. Begin each section on a new page and use both sides of the sheet.*
- 3. Write your candidate-number at the top of each attached sheet.*
- 4. Insert all written foolscaps, graph paper, drawing paper, etc. in their correct sequence and secure with string.*
- 5. For all sheets of paper on which rough/draft work has been done, cross each one through and ATTACH these to your answer scripts.*
- 6. Write clearly the number(s) of the question(s) attempted on the top of each sheet.*
- 7. Show all working clearly where necessary.*
- 8. Programmable calculators are not allowed, especially the ones that do the conversions of number systems.*
- 9. Always check your work before leaving the exam hall.*
- 10. Answer all questions.*

**Section A - Multiple Choice**

[10 marks]

*Choose the appropriate answer from each question by writing the alphabet beside the question number in your answer booklet.*

1. One of the advantages of digital over analog representation is that;
  - A. Data can be processed and transmitted more efficiently and reliably.
  - B. Digital signals typically use less bandwidth.
  - C. Data cannot become corrupted.
  - D. Output is not subject to quantity errors from sampling
  
2. The SOP form of the Boolean expression  $AB + B(CD + EF)$  is;
  - A.  $(A + B)(BCD + BEF)$
  - B.  $AB + BCD + BEF$
  - C.  $(A + B)(B + C + D)(B + E + F)$
  - D.  $AB(B+C+D)(B+E+F)$
  
3. The binary number for  $F7A9_{16}$  is
  - A. 1111011110101001
  - B. 1110111110101001
  - C. 1111111010110001
  - D. 1111011010101001
  
4. What is the weight of digit 6 in the decimal number 1386?
  - A. 1
  - B. 2
  - C. 3
  - D. 0
  
5. The Boolean expression for a 3-input AND gate is;
  - A.  $A + B + C$
  - B.  $ABC$
  - C.  $AB + C$
  - D.  $A \times B + C$
  
6. What is the total number of possible combinations of binary inputs to a gate having three input variables?
  - A. 2
  - B. 4
  - C. 8
  - D. 16

*Please Turn Over*

7. The output of an exclusive-OR gate is HIGH when;


- A. all inputs are LOW
- B. all inputs are HIGH
- C. the inputs are unequal
- D. none of the above

8. How is a J-K flip-flop made to toggle?

- A.  $J = 0, K = 0$
- B.  $J = 1, K = 1$
- C.  $J = 1, K = 0$
- D.  $J = 0, K = 1$

9. Identify the type of Flip Flop the Logic Gate circuit represents;

 - A. MS Flip Flop
- B. SR Flip Flop
- C. T Flip Flop
- D. D Flip Flop



10. The Boolean expression  $A + \bar{B} + C$  is a;

- A. Sum term
- B. Literal term
- C. Product term
- D. Complemented term

## Section B – Number Systems & Logic Gates


[30 marks]

*Show ALL working clearly where required. Answer all questions.*

1. Draw the switch equivalent circuit for an OR Gate. (2 marks)
2. Explain the following threshold voltage acronyms;
  - A.  $V_{IH}$  (1 mark)
  - B.  $V_{OL}$  (1 mark)
3. Convert the decimal number 45.5 to binary by using the sum-of-weights method. (2 marks)

Please Turn Over

 4. Convert the decimal number 57 to the following numbers using any of the conversion methods.
- A. Binary number (2 marks)
  - B. Hexadecimal number (2 marks)
  - C. Octal number (2 marks)
5. Convert the following to octal;
- A.  $3A516_{16}$  (2 marks)
  - B.  $110101111_2$  (2 marks)
6. What is the largest decimal number that can be represented in binary with eight bits? (1 mark)
7. Describe the operation of a 3 input OR gate. (2 marks)
8. Convert the binary number 11000110 to Gray code. (2 marks)
9. What is a Truth Table? Explain clearly. (2 marks)
10. Using the figure below, answer the following questions.



- A. Name the gates labeled G1 and G2. (1 mark)
- B. Draw the truth tables of gates G1 and G2. (2 marks)
- C. Determine the output waveforms X and Y, given the input signals A and B as above. (4 marks)

*Please Turn Over*

**Section C – Boolean Algebra & Logic Simplifications**

[30 marks]

*Show ALL working clearly where required. Answer all questions.*

1. State DeMorgan’s theorem. (2 marks)
2. Convert the Boolean expression,  $\overline{\overline{A+B}+C}$  to SOP form. (2 marks)
3. Apply DeMorgan’s theorem to each expression;
  - A.  $\overline{(A+B+C)D}$  (2 marks)
  - B.  $\overline{\overline{A+B}+C}$  (2 marks)
4. Using Boolean algebra techniques, simplify this expression;
  - A.  $AB+A(B+C)+B(B+C)$  (3 marks)
  - B.  $(A+\overline{B})(A+C)$  (3 marks)
  - C.  $AB+(\overline{A}+\overline{B})C+AB+\overline{BC}$  (2 marks)
5. Draw a truth table for the standard SOP expression;  $\overline{ABC} + \overline{ABC} + ABC$ . (2 marks)
6. Identify the law of Boolean algebra upon which each of the following equalities is based;
  - A.  $\overline{AB}+CD+\overline{ACD}+B = B + \overline{AB} + \overline{ACD}+CD$  (1 mark)
  - B.  $AB(CD+\overline{EF}+GH) = ABCD + ABE\overline{F} + ABGH$  (1 mark)
7. Convert the Boolean expression,  $\overline{ABC} + \overline{AB} + \overline{ABCD}$ , into standard SOP form. (2 marks)
8. What is the minimum POS expression derived from the Karnaugh map shown below? (3 marks)

	YZ	00	01	11	10
WX	00				
01		0	0		
11				0	0
10		0	0	0	0

Please Turn Over


9. Develop a truth table for the POS expression;  $(\bar{A} + \bar{B} + \bar{C})(A + B + C)(A + \bar{B} + C)$   
(2 marks)
10. Use the Karnaugh map to find the minimum SOP form for the expression;  
 $\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}C$ .  
(3 marks)

### Section D – Combinational & Sequential Circuits

[30 marks]

*Show ALL working clearly where required. Answer all questions.*

 1. What do you understand by the term "Positive Edge Triggered Flip-flop"?  
(2 marks)
2. Operating characteristics of flip-flops specify the performance, operating requirements, and operating limitations of the circuit. What do you understand by the following terms that is usually specified in the datasheets of the flip-flops;
  - A. Propagation Delay Time (2 marks)
  - B. Power Dissipation (2 marks)
3. Determine the expression at X for the following circuit.



(2 marks)

4. Flip-flops can be connected together to perform counting operations. Such a group of flip-flops is a counter.
  - A. Draw the circuit of a mod-12 ripple counter using JK Flip-flops for the clock triggering on the rising edge. Show all circuit connections and label the pins clearly. (5 marks)
  - B. Draw the timing diagram for the Q outputs of all flip-flops for twelve clock pulses. (8 marks)

*Please Turn Over*

5. Sensors A, B, and C controls the conveyor belt Q, in a sugar mill. The conveyor must operate if sensor A is ON and B is ON but C is OFF; or if A is OFF, B is ON and C is ON; or if A is ON, B is OFF and C is ON. Under all other conditions the conveyor must NOT operate.
- A. Determine the truth table for all possible combinations of the three sensors. (3 marks)
  - B. Write the Boolean expression for which the conveyor belt is operational. (2 marks)
  - C. Draw the logic circuit to show this operation. Use a LED to indicate the status of the conveyor belt. (4 marks)

The End

-----GOOD LUCK-----

