



COLLEGE OF ENGINEERING, SCIENCE AND TECHNOLOGY

**SCHOOL OF ELECTRICAL & ELECTRONIC
ENGINEERING**

BACHELOR IN ENGINEERING (HONS) (ELECTRICAL & ELECTRONICS)

EEB601 – CIRCUIT THEORY

SEMESTER 1 - 2019. Total [100marks]

DAY/DATE: As per timetable TIME: As per timetable ROOM: As per timetable.

INSTRUCTIONS TO STUDENTS

1. *Candidates are reminded that they should have no books, notes, paper or other material in their possession unless their use is specifically permitted by "instructions to Candidates" set out below.*
2. *Reading time is 10 minutes duration.*
3. *Examination time is of 3 hours duration*
4. *This paper consist of 6 questions, with parts, printed on 8 pages.*
5. *Attempt all 6 questions. Each question may carry a different mark.*
6. *A set of Laplace Transforms Table is attached*
7. *A formula sheet is also attached*
8. *The MatLab software is available on the PC provided.*
9. *Use of the Internet, Google and any other application is strictly prohibited.*
10. *Write your candidate number at the top of each attached sheet*
11. *Start each question on a new page*
12. *Non- programmable Calculators may be used*
13. *Mobile phones are not allowed inside the examination venue.*

FORMULA SHEET

1. $\int u dv = uv - \int v du$
2. Integrating Factor $R = e^{\int P(t) dt}$; $Rf(t) = \int RQ(t) dt$
3. $s = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$
4. $CLTF = \frac{G(s)}{1 + G(s)H(s)}$
5. $f(t) = a_0 + \sum_{n=1}^{\infty} \left(a_n \cos \frac{n\pi}{L} t + b_n \sin \frac{n\pi}{L} t \right)$; $a_0 = \frac{1}{T} \int_0^T f(t) dt = \frac{1}{2L} \int_0^{2L} f(t) dt$;
 $a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega t dt = \frac{1}{L} \int_0^{2L} f(t) \cos \frac{n\pi}{L} t dt$;
 $b_n = \frac{2}{T} \int_0^T f(t) \sin n\omega t dt = \frac{1}{L} \int_0^{2L} f(t) \sin \frac{n\pi}{L} t dt$
6. $q = CV$; $i(t) = \frac{dq}{dt}$; $i(t) = C \frac{dv}{dt}$ $i(t) = \frac{v(t)}{R}$ $w_c = \frac{1}{2} CV^2$
7. $v(t) = L \frac{di}{dt}$; $v(t) = \frac{1}{C} \int i(t) dt$; $v(t) = Ri(t)$; $w_L = \frac{1}{2} LI^2$

EEB601 FINAL EXAMINATION – 2019

QUESTION 1: THEVENIN THEOREM & NORTON THEOREM

[TOTAL: 20]

Q 1 - 1: Thevenin Theorem

Refer to Figure 1. The circuit load is $R_L = 8\Omega$

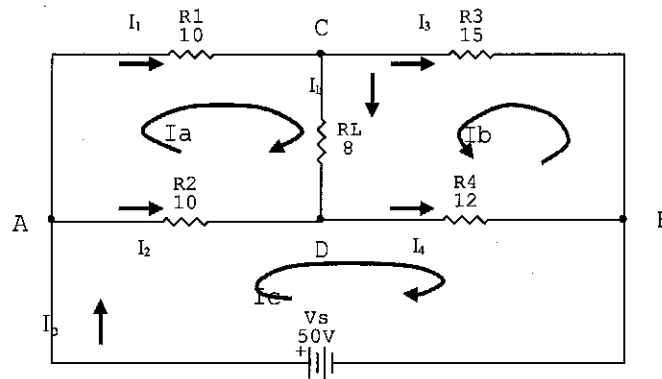


Figure 1: Bridge Network

- (a) Determine the Thevenin equivalent circuit. **[8 marks]**
- (b) Calculate the current through the load, $R_L = 8\Omega$. **[2 marks]**
- (c) Solve for the power absorbed by the load. **[2 marks]**

Q1 - 2: Norton Theorem

Refer to Figure 1.

- (a) Derive the Norton equivalent circuit. **[6 marks]**
- (b) Confirm the current through the load, $R_L = 8\Omega$. **[2 marks]**

QUESTION 2: LOOP ANALYSIS & NODAL ANALYSIS

[TOTAL: 16 MARKS]

Q2 - 1: Loop Analysis

Refer to
Figure 2.

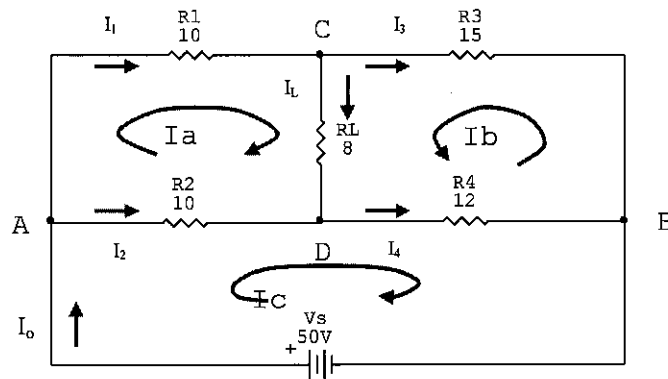


Figure 2: Bridge Network

(a) Solve for the currents I_a , I_b , and I_c . [6 marks]

(b) Work out the current through the load, $R_L = 8\Omega$. [2 marks]

Q2 - 2: Nodal Analysis

(a) Use Nodal Analysis to determine V_C and V_D [6 marks]

(b) Determine the load current, I_L . [2 marks]

EEB601 FINAL EXAMINATION – 2019

QUESTION 3: SUPERPOSITION THEOREM & LOOP ANALYSIS WITH DEPENDENT SOURCE
[TOTAL: 12 MARKS]

Q3-1: Superposition Theorem

Utilize the Superposition Theorem to determine the four unknown currents in Figure 3. Then determine the voltage drop across the 6Ω load. **[8 marks]**

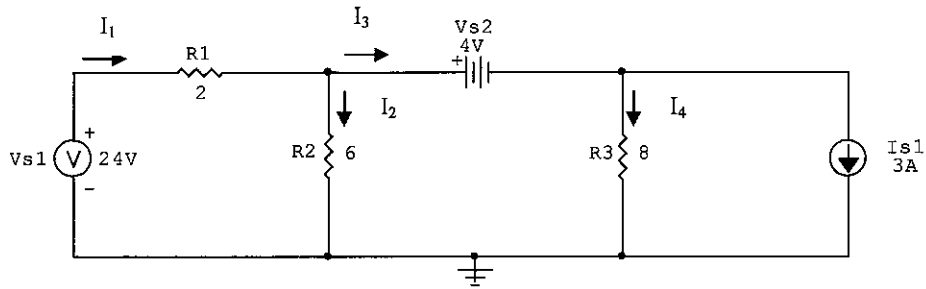


Figure 3

Q3 - 2: Loop Analysis With Dependent Source

Consider Figure 4, shown. Use Loop (Mesh) analysis to determine currents $I_1, I_2, I_3,$ and I_0 . **[4 marks]**

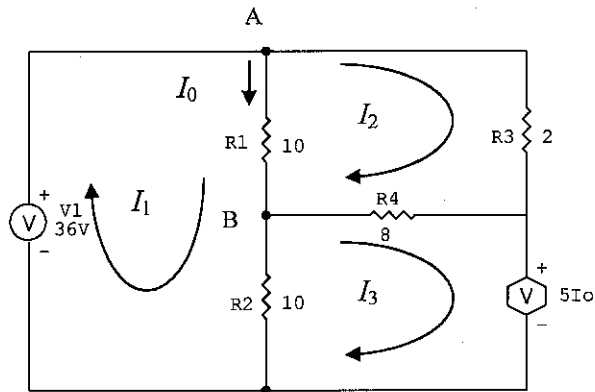


Figure 4

EEB601 FINAL EXAMINATION – 2019

QUESTION 4: SECOND ORDER *RLC* NETWORKS & TRANSIENTS
[TOTAL = 22 MARKS]

Q4 - 1: Analyze the *RLC* Series circuit shown in **Figure 5**. The output is taken across the resistor, *R*. Assume zero initial conditions.

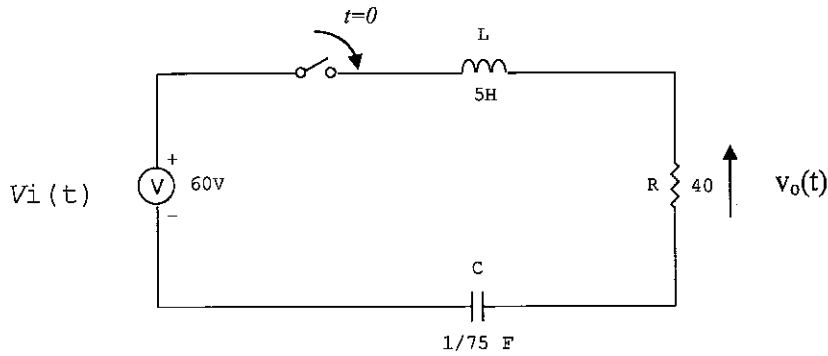


Figure 5: Series *RLC* circuit

- (a) Derive the Second Order Differential Equation model of the system using Kirchhoff's Voltage Law (KVL). **[4 marks]**

- (b) Transform the Differential Equation from time to s-domain using Laplace Transforms, to obtain $Q(s)$ **[5 marks]**

- (c) Determine the Particular Solution $q(t)$ from the $Q(s)$ obtained in (b). **[3 marks]**

[Total: 12 marks]

Q4 - 2: Process the information regarding the Series *RLC* Critically damped circuit shown in **Figure 6**. The initial conditions are $v(0) = 2$ V and $i(0) = 1$ A. Derive the step response $i(t)$ and $v(t)$ for the *RLC* circuit.

[Total: 10 marks]

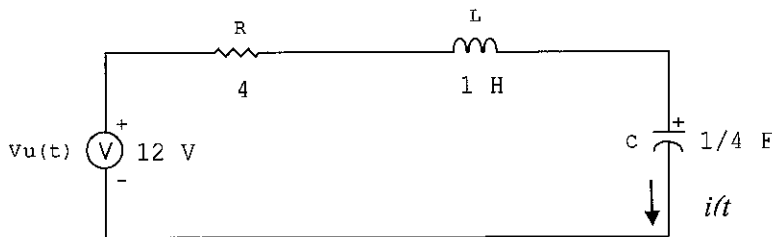


Figure 6: Series *RLC* circuit – Critically damped

EEB601 FINAL EXAMINATION – 2019

QUESTION 5: AC NETWORKS

[TOTAL = 20 MARKS]

Q5-1: A $60\ \Omega$ resistor, a $0.5\ \text{H}$ inductor, and an $8\ \mu\text{F}$ capacitor are connected in series with a $240\ \text{V}$, $60\ \text{Hz}$ ac source.

- (a) Determine the magnitude of the Impedance of the circuit. [3 marks]

- (b) Calculate the effective (rms) current and the phase angle. [3 marks]

- (c) Resolve for the Resonance Frequency. [3 marks]

- (d) Derive the Average Power. [3 marks]

- (e) Analyse for the Power Factor. [2 marks]

Q5 - 2: A balanced Δ -connected load having an impedance $20-j15\ \Omega$ is connected to a Δ -connected positive-sequence generator having $V_{ab} = 330\angle 0^\circ\ \text{V}$. Calculate the phase currents of the load and the line currents. [6 marks]

QUESTION 6: TWO-PORT NETWORKS [TOTAL: 10 MARKS]

Q6 - 1: Determine the Z-parameters of the circuit in Figure 7 given the relationships stated. [6 marks]

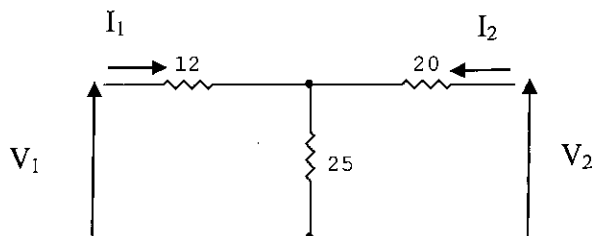


Figure 7

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

EEB601 FINAL EXAMINATION – 2019

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

Q6 – 2: Analyse for the Z-parameters for the circuit of Figure 8.

[4 marks]

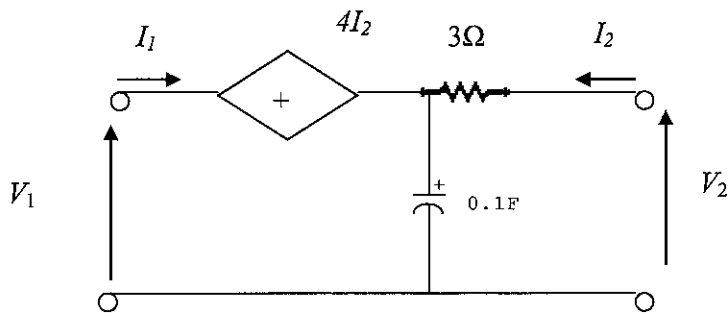


Figure 8

[END OF EXAMINATION]

TABLE OF LAPLACE TRANSFORMS

$F(s) = L[f(t)]$	$f(t), t \geq 0$
1. 1	$\delta(t_0)$, Unit Impulse at $t = t_0$
2. $\frac{1}{s}$	1, Unit Step
3. $\frac{n!}{s^{n+1}}$	t^n
4. $\frac{1}{s+a}$	e^{-at}
5. $\frac{1}{(s+a)^n}$	$\frac{1}{(n-1)!} t^{n-1} e^{-at}$
6. $\frac{a}{s(s+a)}$	$1 - e^{-at}$
7. $\frac{1}{(s+a)(s+b)}$	$\frac{1}{(b-a)} (e^{-at} - e^{-bt})$
8. $\frac{s+\alpha}{(s+a)(s+b)}$	$\frac{1}{(b-a)} [(\alpha-a)e^{-at} - (\alpha-b)e^{-bt}]$
9. $\frac{ab}{s(s+a)(s+b)}$	$1 - \frac{b}{(b-a)} e^{-at} + \frac{a}{(b-a)} e^{-bt}$
10. $\frac{1}{(s+a)(s+b)(s+c)}$	$\frac{e^{-at}}{(b-a)(c-a)} + \frac{e^{-bt}}{(c-a)(a-b)} + \frac{e^{-ct}}{(a-c)(b-c)}$
11. $\frac{s+\alpha}{(s+a)(s+b)(s+c)}$	$\frac{(\alpha-a)e^{-at}}{(b-a)(c-a)} + \frac{(\alpha-b)e^{-bt}}{(c-b)(a-b)} + \frac{(\alpha-c)e^{-ct}}{(a-c)(b-c)}$
12. $\frac{ab(s+\alpha)}{s(s+a)(s+b)}$	$\alpha - \frac{b(\alpha-a)}{(b-a)} e^{-at} + \frac{a(\alpha-a)}{(b-a)} e^{-bt}$
13. $\frac{\omega}{s^2 + \omega^2}$	$\sin \omega t$
14. $\frac{s}{s^2 + \omega^2}$	$\cos \omega t$
15. $\frac{s+a}{s^2 + \omega^2}$	$\frac{\sqrt{\alpha^2 + \omega^2}}{\omega} \sin(\omega t + \phi),$ $\phi = \tan^{-1}\left(\frac{\omega}{\alpha}\right)$
16. $\frac{\omega}{(s+a)^2 + \omega^2}$	$e^{-at} \sin \omega t$

TABLE OF LAPLACE TRANSFORMS

$$F(s) = L[f(t)]$$

$$f(t), t \geq 0$$

$$17. \frac{(s+a)}{(s+a)^2 + \omega^2}$$

$$e^{-at} \cos \omega t$$

$$18. \frac{s+\alpha}{(s+a)^2 + \omega^2}$$

$$\frac{1}{\omega} [(\alpha - a)^2 + \omega^2]^{\frac{1}{2}} e^{-at} \sin(\omega t + \phi),$$

$$\phi = \tan^{-1} \left(\frac{\omega}{\alpha - a} \right)$$

$$19. \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\frac{\omega_n}{\sqrt{1-\zeta^2}} e^{-\zeta\omega_n t} \sin \omega_n \sqrt{1-\zeta^2} t, \zeta < 1$$

$$20. \frac{1}{s[(s+a)^2 + \omega^2]}$$

$$\frac{1}{a^2 + \omega^2} + \frac{1}{\omega \sqrt{a^2 + \omega^2}} e^{-at} \sin(\omega t - \phi),$$

$$\phi = \tan^{-1} \left(\frac{\omega}{-a} \right)$$

$$21. \frac{\omega_n^2}{s(s^2 + 2\zeta\omega_n s + \omega_n^2)}$$

$$1 - \frac{1}{\sqrt{1-\zeta^2}} e^{-\zeta\omega_n t} \sin(\omega_n \sqrt{1-\zeta^2} t + \phi),$$

$$\phi = \cos^{-1} \zeta, \zeta < 1$$

$$22. \frac{(s+\alpha)}{s[(s+a)^2 + \omega^2]}$$

$$\frac{\alpha}{a^2 + \omega^2} + \frac{1}{\omega} \left[\frac{(\alpha - a)^2 + \omega^2}{a^2 + \omega^2} \right]^{\frac{1}{2}} e^{-at} \sin(\omega t + \phi),$$

$$\phi = \tan^{-1} \left(\frac{\omega}{\alpha - a} \right) - \tan^{-1} \left(\frac{\omega}{-a} \right)$$

$$23. \frac{1}{(s+c)[(s+a)^2 + \omega^2]}$$

$$\frac{e^{-ct}}{(c-a)^2 + \omega^2} + \frac{e^{-at} \sin(\omega t + \phi)}{\omega [(c-a)^2 + \omega^2]^{\frac{1}{2}}},$$

$$\phi = \tan^{-1} \left(\frac{\omega}{c-a} \right)$$

TABLE OF LAPLACE TRANSFORMS

24.	$\frac{a}{s^2 - a^2}$	$\sinh at$
25.	$\frac{s}{s^2 - a^2}$	$\cosh at$
26.	$\frac{\omega^2}{s(s^2 + \omega^2)}$	$1 - \cos \omega t$
27.	$\frac{\omega^3}{s^2(s^2 + \omega^2)}$	$\omega t - \sin \omega t$
28.	$\frac{2\omega^3}{(s^2 + \omega^2)^2}$	$\sin \omega t - \omega t \cos \omega t$

TABLE OF LAPLACE TRANSFORMS

$$F(s) = L[f(t)] \qquad f(t), \quad t \geq 0$$

29. $\frac{s}{(s^2 + \omega^2)^2}$ $\frac{t}{2\omega} \sin \omega t$
30. $\frac{s^2}{(s^2 + \omega^2)^2}$ $\frac{1}{2\omega} (\sin \omega t + \omega t \cos \omega t)$
31. $\frac{s}{(s^2 + a^2)(s^2 + b^2)} \quad (a^2 \neq b^2)$ $\frac{1}{b^2 - a^2} (\cos at - \cos bt)$

LAPLACE TRANSFORM OF DERIVATIVES

32. $sF(s) - f(0)$ $f'(t)$, First Derivative
33. $s^2 F(s) - sf(0) - f'(0)$ $f''(t)$, Second Derivative

GENERAL PROPERTIES OF LAPLACE TRANSFORMS

1. Linearity $L[af_1(t) + bf_2(t)] = aF_1(s) + bF_2(s)$
2. Scaling $L[f(at)] = \frac{1}{a} F\left(\frac{s}{a}\right)$
3. Transform of a Derivative $L[f^{(n)}(t)] = s^n F(s) - s^{n-1} f(0) - s^{n-2} f'(0) - \dots - sf^{(n-2)}(0) - f^{(n-1)}(0)$
4. First Shifting Theorem $L[e^{at} f(t)] = F(s - a)$
(Complex Translation; s -shifting)
5. Second Shifting Theorem $L[u(t - a) f(t - a)] = e^{-as} F(s)$
(Real Translation; t -shifting)
6. Integration $L\left[\int_0^t f(\tau) d\tau\right] = \frac{1}{s} F(s)$
7. Complex Differentiation $L[tf(t)] = -\frac{dF(s)}{ds}$
8. Final Value Theorem $f(\infty) = \lim_{s \rightarrow 0} sF(s)$
9. Initial Value Theorem $f(0+) = \lim_{s \rightarrow \infty} sF(s)$