



COLLEGE OF ENGINEERING, SCIENCE & TECHNOLOGY  
SCHOOL OF ELECTRICAL & ELECTRONIC

ENGINEERING

TRADE DIPLOMA IN ELECTRICAL ENGINEERING  
STAGE 4

EEE535–ELECTRO- TECHNOLOGY

SEMESTER 1 - 2019.

Total marks-100%-----Duration: 3Hrs 10 Minutes

DAY/DATE: \_\_\_\_\_ TIME: \_\_\_\_\_ ROOM: As per timetable.


**INSTRUCTIONS TO STUDENTS**

1. *You are allowed 10 minutes Extra reading time during which you are NOT to write.*
2. *Begin each answer on a fresh page and use both sides of the sheet.*
3. *Write your candidate-number at the top of each attached sheet.*
4. *Insert all written sheets in their correct sequence and secure with string.*
5. *For all sheets of paper on which rough/draft work has been done, cross it though and you MUST ATTACH to your answer scripts.*
6. *Write clearly the number(s) of the question(s) attempted on the top of each sheet.*
7. *Answer all Questions*
8. *Show all workings where necessary.*
9. *Do not use programmable calculators, especially the ones that does the conversions of number systems.*
10. ***CHECK YOUR WORK BEFORE YOU LEAVE THE ROOM!***

*Attempt all the questions*

**Question 1**

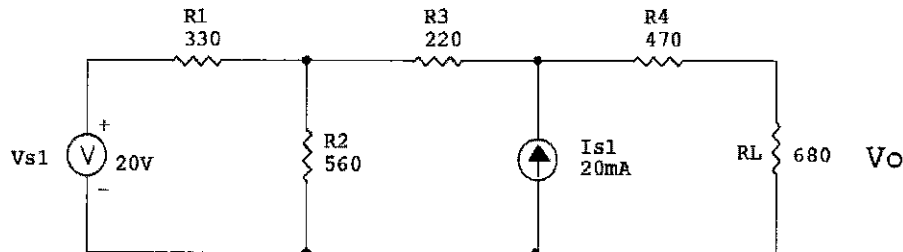a) Reduce the circuit shown to its Thevenin and Norton equivalent circuits. (15 marks)




b) Find the value of  $R_L$  for maximum power transfer in the circuit (5 marks)

c) Find the maximum power. (5 marks)

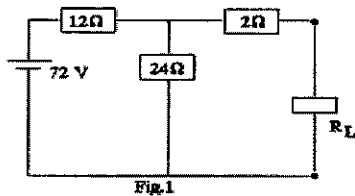**Question 2**

For the circuit shown in Fig. 1, find the value of  $R_L$  for maximum power transfer.



(5 marks)


**Question 3**

A coil of inductance 318.3mH and negligible resistance is connected in series with a 200 $\Omega$  resistor to a 240V, 50 Hz supply. Calculate the p.d. across each component.

(5 marks)

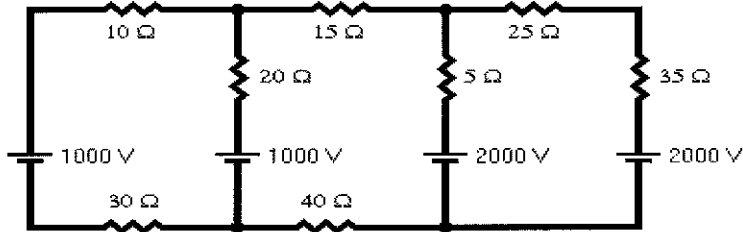**Question 4**


Use nodal analysis to find the voltage at each node of this circuit.



(10 marks)

**Question 5**

Execute  $Y \rightarrow \Delta (R_{ab})$

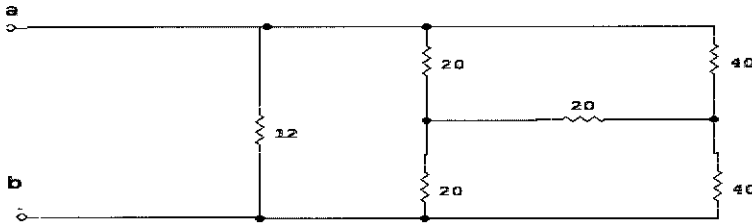


(10 marks)

**Question 6**


a) Given the following circuit. Determine the Z parameters

(10 marks)

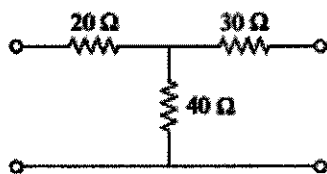


b) Obtain hybrid parameters for the network shown

(10 marks)

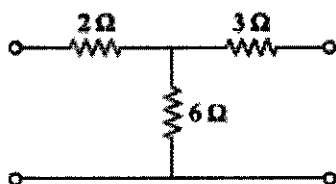

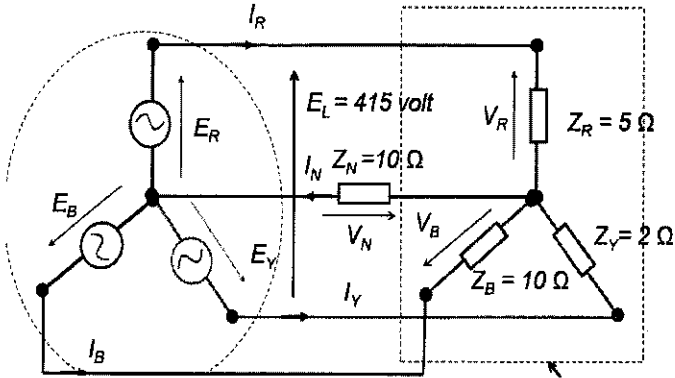**Question 7**

Find line currents  $I_R$ ,  $I_Y$ ,  $I_B$  and  $I_N$  for the circuit given below



(10 marks)

**Question 8**

Determine the Laplace Transform of each of the following functions.

a)  $t^2 - 2t$

(1marks)

b)  $\cos wt$

(2 marks)

c)  $e^{at} \cos wt$

(2 marks)

**Question 9**

a) Find the inverse Laplace transform of  $F(s) = \frac{1}{s + 2}$

(5 marks)

b) Find the Laplace transform of  $\int_0^t \sin(at) \cos(at) dt$

(5marks)

-----THE END-----

TABLE

	$f(t)$	$\mathcal{L}[f(t)] = \mathcal{L}(f)$
1.	1	$\frac{1}{s}$
2.	t	$\frac{1}{s^2}$
3.	$t^2$	$\frac{2!}{s^3}$
4.	$t^n$	$\frac{n!}{s^{n+1}}$
5.	$e^{at}$	$\frac{1}{s-a}$
6.	$\cos wt$	$\frac{s}{s^2+w^2}$
7.	$\sin wt$	$\frac{w}{s^2+w^2}$
8.	$\cosh at$	$\frac{s}{s^2-a^2}$
9.	$\sinh at$	$\frac{a}{s^2-a^2}$
10.	$e^{at} \cos wt$	$\frac{s-a}{(s-a)^2+w^2}$
11.	$e^{at} \sin wt$	$\frac{w}{(s-a)^2+w^2}$
12.	$t^a (a > 0)$	$\frac{\Gamma(a+1)}{s^{a+1}}$

